

ECE159H1: Fundamentals of Electric Circuits


Midterm – Thursday March 2, 2023

Solutions


- Make sure to **accurately** enter your first name, last name, and student number above.
- The Midterm is worth 80 marks and has four questions. Each question is worth 20 marks.
- Show all of your work, and the final page is left blank which you can use for rough work or for extra space for your answers.
- Take a deep breath and relax 😊.

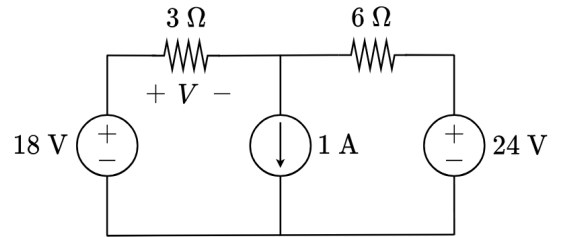Question #1 (20 marks)

- (8 marks) 1. (a) For the circuit shown, find the voltage V using superposition and the voltage/current division rules.




Source #1:

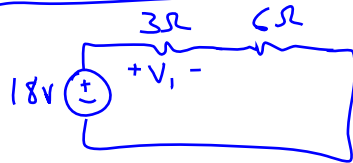

$$V_1 = 18 \left(\frac{3}{3+6} \right) = \frac{18}{3} = \underline{6V}$$


Source #2:

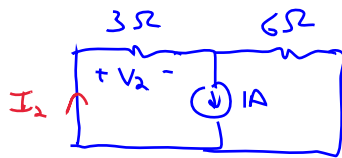

$$I_2 = (1) \left(\frac{6}{3+6} \right) = \frac{6}{9} = \frac{2}{3} A$$

$$\therefore V_2 = (3) \left(\frac{2}{3} \right) = \underline{2V}$$

Source #3:

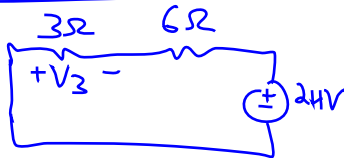



$$V_3 = -24 \left(\frac{3}{6+3} \right) = \frac{-24}{3} = \underline{-8V}$$

negative due to the opposite polarity of the 24V source and how V is defined

Total V : $V = V_1 + V_2 + V_3 = 6 + 2 - 8 = \underline{\underline{0V}}$

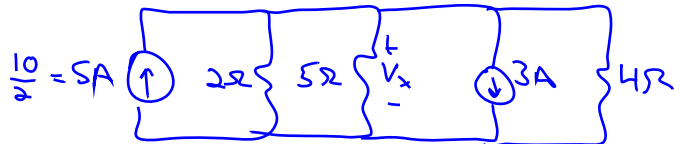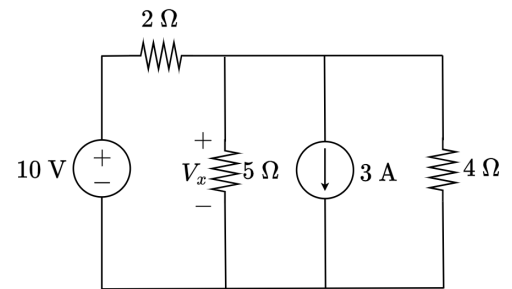Question #1 (cont'd)

- (6 marks) 1. (b) In the circuit shown to the right, find the voltage V_x using source transformation.



Combining sources and simplifying leads to:




$$I_x = 2 \left(\frac{4/3}{4/3 + 5} \right) = \frac{8}{19} \text{ A}$$

$$\therefore V_x = 5I_x = \frac{40}{19} \text{ A} \approx \underline{\underline{2.105 \text{ A}}}$$

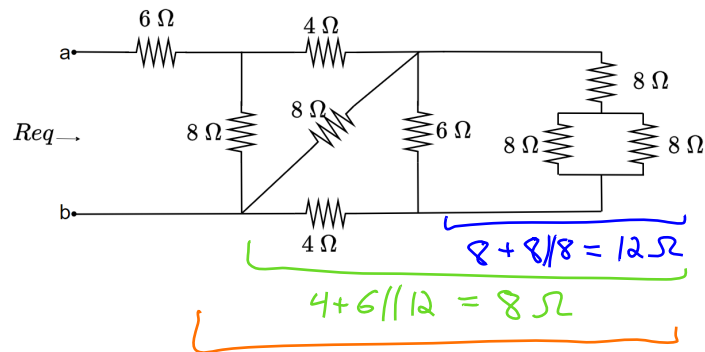Question #1 (cont'd)

- (6 marks) 1. (c) For the combination of resistors shown below, find the equivalent resistance (R_{eq}) between terminals a-b. Clearly indicate the steps you take to find this equivalent resistance.



$$\therefore R_{eq} = 6\Omega + 4\Omega$$


$$= \underline{\underline{10\Omega}}$$

Question #2 (20 marks)

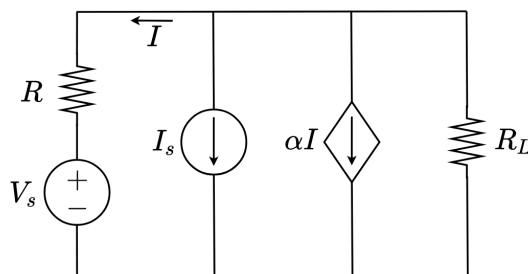2. In the circuit given below,


- (12 marks) (a) Find the Thévenin equivalent circuit seen by the resistor R_L .
 (2 marks) (b) Find R_L such that the maximum power is delivered to R_L .
 (6 marks) (c) Derive an expression for the maximum transferrable power to R_L in terms of R , V_S , I_S , and α .

You may assume that α is a positive constant.



(a)

For V_{oc} :

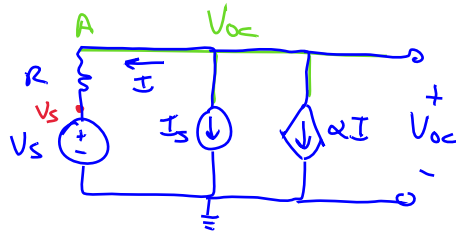

$$\text{KVL @ A: } \frac{V_{oc} - V_S}{R} + I_S + \alpha I = 0$$


$$\text{But } I = \frac{V_{oc} - V_S}{R}$$

$$\therefore (1 + \alpha) \left(\frac{V_{oc} - V_S}{R} \right) + I_S = 0$$

$$V_{oc} \left(\frac{1 + \alpha}{R} \right) = -I_S + V_S \left(\frac{1 + \alpha}{R} \right)$$

$$V_{oc} = V_S - \left(\frac{R}{1 + \alpha} \right) I_S$$

For R_{th} :

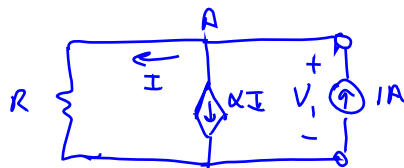

$$R_{th} = \frac{V_1}{1A} \rightarrow \text{need to find } V_1$$

$$\text{KCL @ A: } 1 = \alpha I + I = (\alpha + 1)I \rightarrow I = \frac{1}{1 + \alpha}$$

$$V_1 = IR = \frac{R}{1 + \alpha}$$

$$\therefore R_{th} = \frac{V_1}{1} = \frac{R}{1 + \alpha}$$

\therefore The Thévenin Equivalent is:



Question #2 (cont'd)

(b) For maximum power transfer $R_L = R_{Th} = \underline{\underline{\frac{R}{1+\alpha}}}$

$$\begin{aligned} \text{(c) } P_{max} &= \frac{V_{oc}^2}{4R_{Th}} = \frac{\left[V_s - \left(\frac{R}{1+\alpha} \right) I_s \right]^2}{4 \left(\frac{R}{1+\alpha} \right)} \\ &= \frac{V_s^2 - 2V_s I_s \left(\frac{R}{1+\alpha} \right) + \left(\frac{R}{1+\alpha} \right)^2 I_s^2}{4 \left(\frac{R}{1+\alpha} \right)} \\ &= \underline{\underline{\frac{V_s^2}{4} \left(\frac{1+\alpha}{R} \right) - \frac{V_s I_s}{2} + \frac{I_s^2}{4} \left(\frac{R}{1+\alpha} \right)}} \end{aligned}$$

Question #3 (20 marks)


3. In the circuit below, use Nodal Analysis or Mesh Analysis to find:

(15 marks)

(a) The voltage V_x and the current I_x

(5 marks)

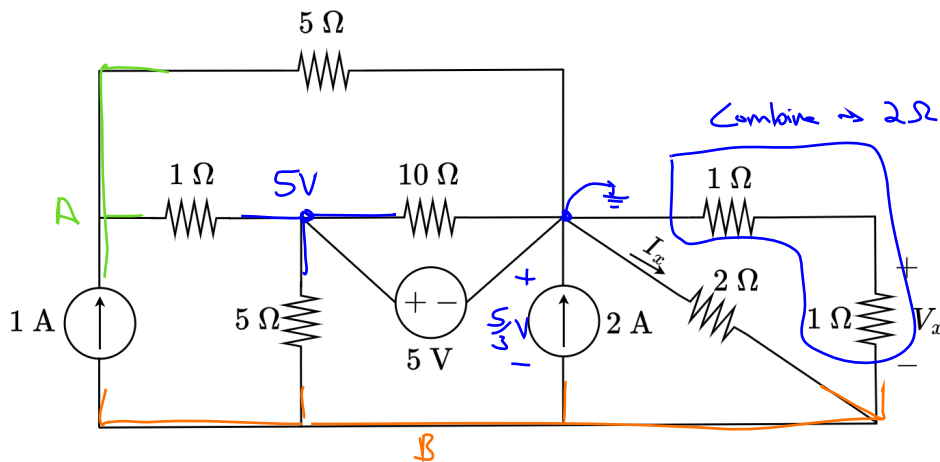(b) The power supplied by the 2 A current source



(a) Using Nodal Analysis: 2 unknowns, V_A & V_B

↳ However, we only need to find V_B to find V_x & I_x

$$\text{KCL @ B: } 10\left(1 + \frac{V_B - 5}{5}\right) + 2 + \frac{V_B}{2} + \frac{V_B}{2} = (0)10$$

$$10 + 2V_B - 10 + 20 + 5V_B + 5V_B = 0 \rightarrow V_B = \frac{-20}{12} = \underline{\underline{-\frac{5}{3} \text{ V}}}$$

$$\therefore I_x = \frac{-V_B}{2} = \underline{\underline{\frac{5}{6} \text{ A}}} \quad V_x = -V_B \left(\frac{1}{1+1}\right) = \left(\frac{5}{3}\right)\left(\frac{1}{2}\right) = \underline{\underline{\frac{5}{6} \text{ V}}}$$

(b) Since the 2A source leaves the positive terminal of the voltage across this current source \rightarrow the source is supplying power.

$$P_{2A} = -\left(\frac{5}{3}\right)(2) = \underline{\underline{-\frac{10}{3} \text{ W}}} \quad (\text{supplying})$$

↳ This is negative since it is supplying power.

Question #4 (20 marks)

4. For the op-amp circuit shown below:

(12 marks)

(a) Determine the values of R and R_0 that will produce an output voltage given by:

$$V_o = 160I_S - \frac{1}{9}V_S$$

(8 marks)

(b) Calculate the percentage of the power dissipated in the circuit's 5 resistors that is provided by the two sources V_S and I_S . Briefly justify your answer. For this part (b), you can assume that $R = 150 \Omega$ and $R_0 = 50 \Omega$, and that the sources have the values of $V_S = 18 \text{ V}$ and $I_S = 90 \text{ mA}$.

You can use the ideal model for the op-amp for both parts of this question.

Soln #1

(a) KVL @ A:

$$R R_0 \left(\frac{V_S - I_S R}{R} \right) = \left(\frac{I_S R - V_o}{R} + \frac{I_S R - V_o}{R_0} \right) R R_0$$

$$R_0 V_S - I_S R R_0 = I_S R R_0 - R V_o + I_S R^2 - R V_o$$

$$V_o (R + R_0) = (R^2 + 2R R_0) I_S - R_0 V_S$$

$$\therefore V_o = \frac{R(R + 2R_0)}{R + R_0} I_S - \frac{R_0}{R + R_0} V_S$$

$$\text{For } V_o = 160 I_S - \frac{1}{9} V_S$$

$$\frac{R(R + 2R_0)}{R + R_0} = 160 \quad \text{and} \quad \frac{R_0}{R + R_0} = \frac{1}{9} \quad (2)$$

$$R + R_0 = 9 R_0$$


$$R = 8 R_0 \quad (3)$$

$$(3) \rightarrow (1) \quad \frac{8 R_0 (8 R_0 + 2 R_0)}{8 R_0 + R_0} = 160$$

$$80 R_0 = 160(9) = 1440$$

$$R_0 = \frac{1440}{80} = \underline{\underline{18 \Omega}} \quad (4)$$
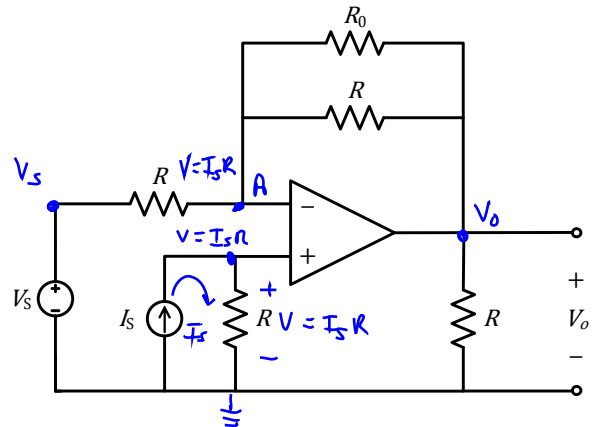
$$(4) \rightarrow (3) \quad R = 8(18) = \underline{\underline{144 \Omega}}$$



(a) Soln #2: Inv. & Non-Inv. configurations and superposition

Inv. Output

$$V_{o1} = - \left(\frac{R_0 // R}{R} \right) V_S = - \left(\frac{R_0}{R + R_0} \right) V_S$$

Non-Inv. Output Input voltage at two terminals

$$\begin{aligned} V_{o2} &= \left(1 + \frac{R // R_0}{R} \right) I_S R = \left(R + \frac{R R_0}{R + R_0} \right) I_S \\ &= \left[\frac{R(R + R_0) + R R_0}{R + R_0} \right] I_S \\ &= \frac{R(R + 2R_0)}{R + R_0} I_S \end{aligned}$$

$$\therefore V_o = V_{o1} + V_{o2}$$

$$= \frac{R(R + 2R_0)}{R + R_0} I_S - \frac{R_0}{R + R_0} V_S$$

For $V_o = 160 I_S - \frac{1}{9} V_S$ we can solve and find that $R = \underline{\underline{144 \Omega}}$ & $R_0 = \underline{\underline{18 \Omega}}$

Question #4 (cont'd)

(b) With $V_S = 18V$, $I_S = 90mA$, $R = 150\Omega$, $R_o = 50\Omega$:

$$V_o = \frac{R(R+2R_o)}{R+R_o} I_S - \frac{R_o}{R+R_o} V_S = 187.5(0.09) - \frac{1}{4}(18) \\ = \underline{12.375 V}$$

The power dissipated by the circuits 5 resistors is:

$$P_{diss} = I_S^2 R + \frac{(V_S - I_S R)^2}{R} + \frac{(I_S R - V_o)^2}{R} + \frac{(I_S R - V_o)^2}{R_o} + \frac{V_o^2}{R} \\ = 1.215 + 0.135 + 0.00844 + 0.0253125 + 1.0269375 \\ = \underline{2.405 W}$$

The power supplied by the sources:

$$P_{supp} = V_S \left(\frac{V_S - I_S R}{R} \right) + I_S (I_S R) \\ = 0.54 + 1.215 = \underline{1.755 W}$$

\therefore The percentage of dissipated power supplied by the sources is $\frac{\text{Power supplied}}{\text{Power dissipated}} = \frac{1.755W}{2.405W} = 73\%$ $\left(\frac{P_{diss}}{P_{supp}} = 137\% \text{ is also acceptable} \right)$

This makes sense as the op-amp DC sources will provide the other 27% of this dissipated power.