

University of Toronto
FACULTY OF APPLIED SCIENCE AND ENGINEERING

FINAL EXAM

April 21st, 2022

150 minutes

First Year – Engineering Science

ECE159S – ELECTRIC CIRCUIT FUNDAMENTALS

Exam Type: A

Calculator Type: 2

Examiners: A. Hooshyar, R. Paranjape

Name:

[Redacted]

First

[Redacted]

Last

Please write your name and student number on Page 2 as well.

SECTION (circle one):

LEC101 (Paranjape)

LEC102 (Hooshyar)

INSTRUCTIONS:

- This is a Type A examination, i.e., no aids except for non-programmable calculators are allowed.
- This exam has five questions and 28 pages.
- All work is to be done on the pages of this booklet.
- When answering the questions, include all the steps of your work on these pages. In addition, place the answers in the provided boxes that are located next to each question.
- Do not unstaple this exam booklet.


| | |
|-------|-----------|
| Q1 | 10 /15 |
| Q2 | 17.5 /25 |
| Q3 | 17 /20 |
| Q4 | 20 /20 |
| Q5 | 18 /20 |
| Total | 82.5 /100 |

1. In the circuit below, for $t < 0$, switch S_1 has been at position A, and switch S_2 has been open. At $t = 0$ s, switch S_1 is moved from position A to position B. At $t = 0.1$ s, switch S_2 is closed. Find $i_o(t)$ and $i_1(t)$ for $t > 0$.


$$v(t) = v_o + (v(\infty) - v_o) e^{-t/\tau}$$

$$i(t) = i_o + (i(\infty) - i_o) e^{-t/\tau}$$

| | |
|---------------|--|
| $0 < t < 0.1$ | $i_o(t) = 6.67 \times 10^{-4} + (1.15 \times 10^{-4}) e^{-\frac{t}{1.22 \times 10^{-6}}} \text{ A}$ |
| $t > 0.1$ | $i_o(t) = 7.82 \times 10^{-4} - 5.6 \times 10^{-4} e^{-\frac{(t-0.1)}{1.22 \times 10^{-6}}} \text{ A}$ |
| $0 < t < 0.1$ | $i_1(t) = 0 \text{ A}$ ✓ |
| $t > 0.1$ | $i_1(t) = \frac{1}{2000} e^{-(t-0.1)/3.33 \times 10^{-6}} \text{ A}$ |

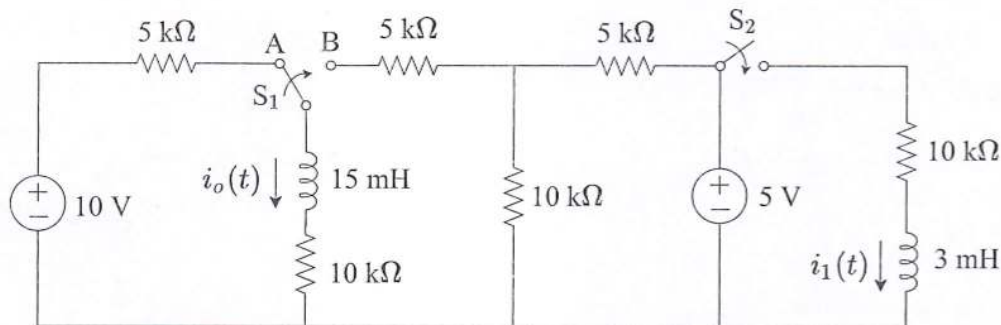

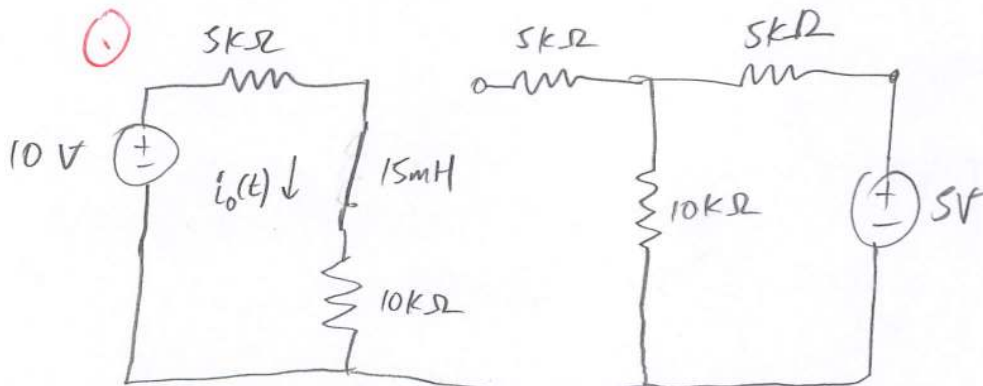for $t < 0$; steady state DC cond; open cap short ind.




(1) $i_1(t) = 0$
since open.
 $\therefore i_1(0) = 0.$

$i_o(t)$: KVL: $-10 + 5000i_o + 10000i_o = 0.$

$i_o = 6.67 \times 10^{-4} \text{ A.}$ (1)

$\therefore i_o(0) = 6.67 \times 10^{-4} \text{ A.} = 0.667 \text{ mA.}$ (1)


for $t > 0, t < 0.1$:

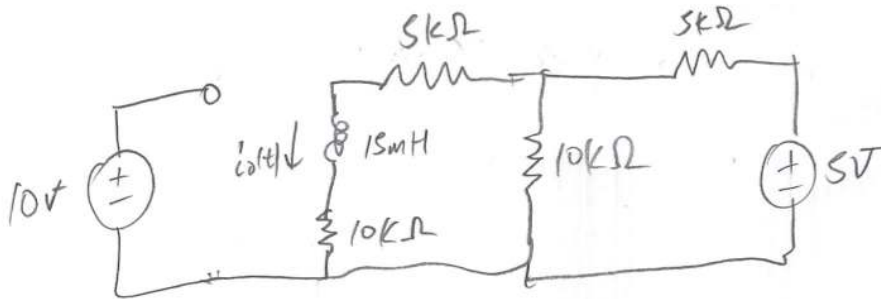


$$i_1(t) = 0 \text{ (open)}$$

find R_{th} & $i_o(\infty)$:

R_{th} method 1

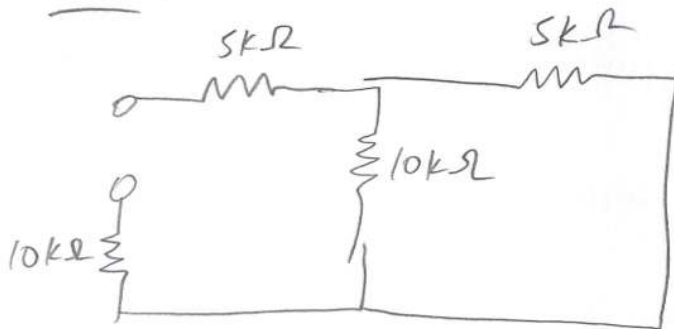


\Rightarrow

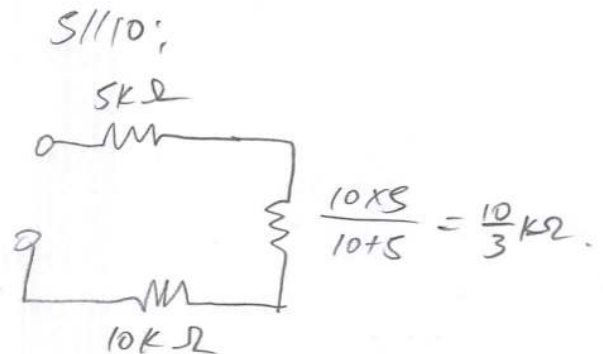

$$\Rightarrow R_{th} = 5 + \frac{10}{3} + 10 = \frac{55}{3} k\Omega$$

$i_o(\infty)$: Steady state DC:

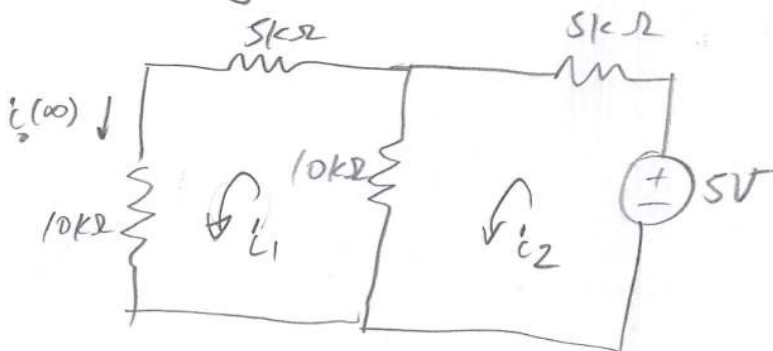

loop ①:

$$10i_1 + 10(i_1 - i_2) + 5i_1 = 0$$

loop ②:

$$-5 + 5i_2 + 10(i_2 - i_1) = 0$$

$$\Rightarrow 25i_1 - 10i_2 = 0$$

$$-10i_1 + 15i_2 = 5$$

$$i_1 = \frac{2}{11} mA \Rightarrow i_o(\infty) = \frac{2}{11} mA = \frac{2}{11} \times 10^{-3} A$$

∴ for this interval:

$$i_o(t) = 6.67 \times 10^{-4} + \left(\frac{2}{11} \times 10^{-3} - 1 \right) e^{-\frac{t}{(55/3 \times 10^3 / 15 \times 10^{-3})}} \quad \text{A}$$

$$= 6.67 \times 10^{-4} + (1.1515 \times 10^{-4}) e^{-\frac{t}{1.222 \times 10^{-6}}} \quad \text{A.}$$


$$i_1(t) = 0. \quad (-1)$$

⇒ int: $i_o(0.1) = 7.8215 \times 10^{-4} \text{ A.}$
 $i_1(0.1) = 0$

$t > 0.1$;

And R_{th} , R_{th} , $i_1(\infty)$, $i_o(\infty)$

$i_o, i_1 @ \infty$

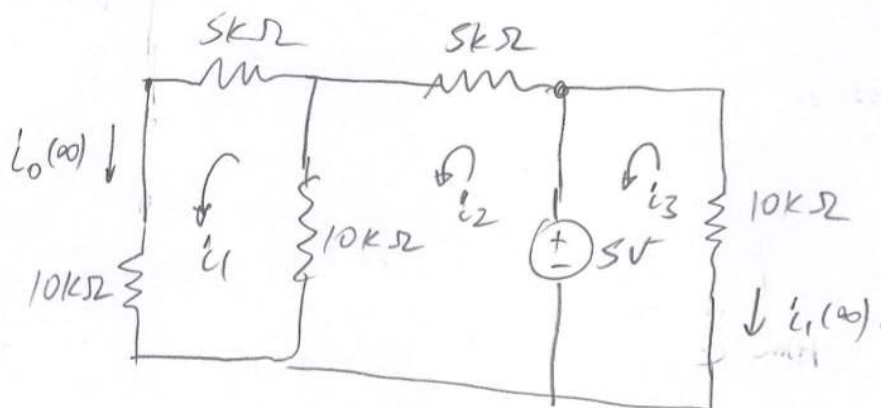

$$\begin{aligned} \text{loop 1: } 5i_1 + 10i_1 + 10(i_1 - i_2) &= 0 & (5+10+10)i_1 - 10i_2 &= 0 \\ \text{loop 2: } 10(i_2 - i_1) - 5 + 5(i_2) &= 0 & (-10)i_1 + (10+5)i_2 &= 5 \\ \text{loop 3: } +5 + 10i_3 &= 0 & \rightarrow i_3 &= -\frac{1}{2} \text{ mA.} \end{aligned}$$

$$i_1 = \frac{5}{23} \text{ mA}$$



$$i_o(\infty) = \frac{5}{23} \text{ mA}$$

$$i_2 = \frac{11}{23} \text{ mA}$$


$$i_1(\infty) = \frac{1}{2} \text{ mA. } \textcircled{1}$$

R_{th1} , R_{th2} :

for $i_o(t)$, method 1 @ DC behaviour;

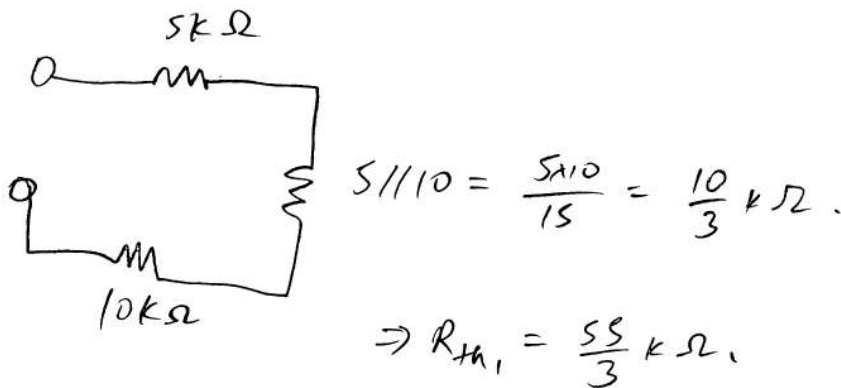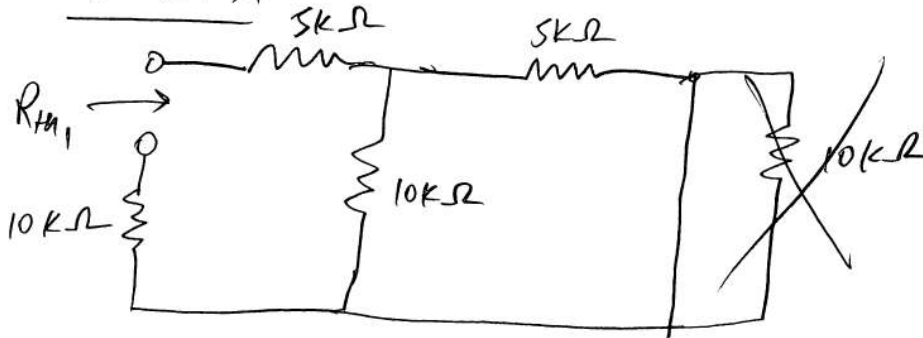

for $i_o(t)$, method 1; DC;

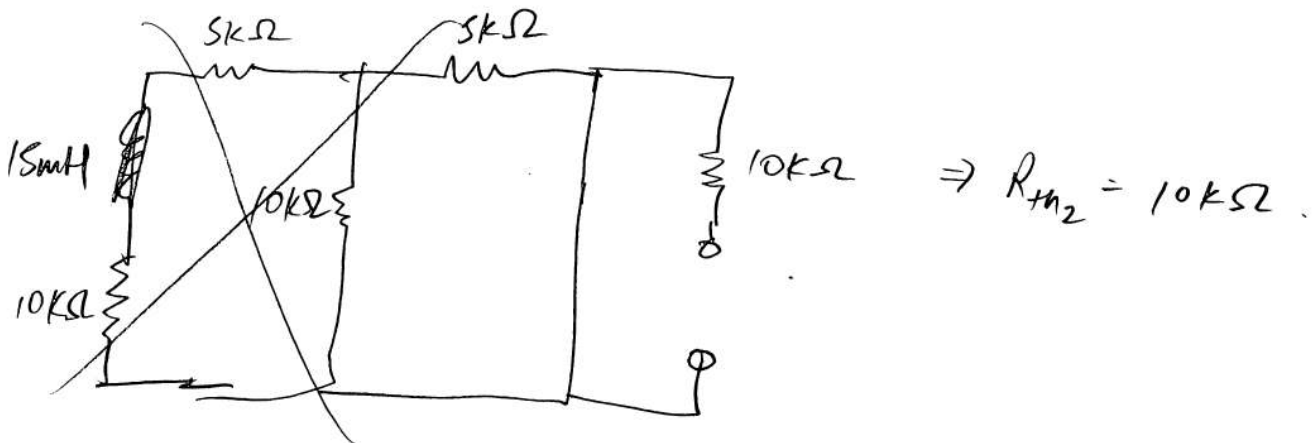

$$\Rightarrow i_o(0.1) = 7.8215 \times 10^{-4} \text{ A} = 0.782 \text{ mA}.$$

$$i_1(0.1) = 0.$$

$$R_{Th1} = \frac{55}{3} \text{ k}\Omega.$$

$$R_{Th2} = 10 \text{ k}\Omega.$$

$$i_o(\infty) = \frac{5}{23} \text{ mA}$$

$$i_1(\infty) = \frac{1}{2} \text{ mA}.$$

$$\text{So, } i_o(t) = 7.8215 \times 10^{-4} + \left(\frac{5}{23} \times 10^{-3} - 7.8215 \times 10^{-4} \right) e^{\frac{-(t-0.1)}{55/3 \times 10^3 / 15 \times 10^{-3}}}$$

$$i_1(t) = 0 + \left(\frac{1}{2} \times 10^{-3} - 0 \right) e^{\frac{-(t-0.1)}{10000/3 \times 10^{-3}}}$$

$$\Rightarrow i_o(t) = 7.8215 \times 10^{-4} - 5.647 \times 10^{-4} e^{\frac{-(t-0.1)}{1.22 \times 10^6}} \text{ A}.$$

$$i_1(t) = \frac{1}{2000} e^{\frac{-(t-0.1)}{3.33 \times 10^6}} \text{ A}.$$

Q 2


(1) R_{Th}

(2) $i_1(t)$

Super

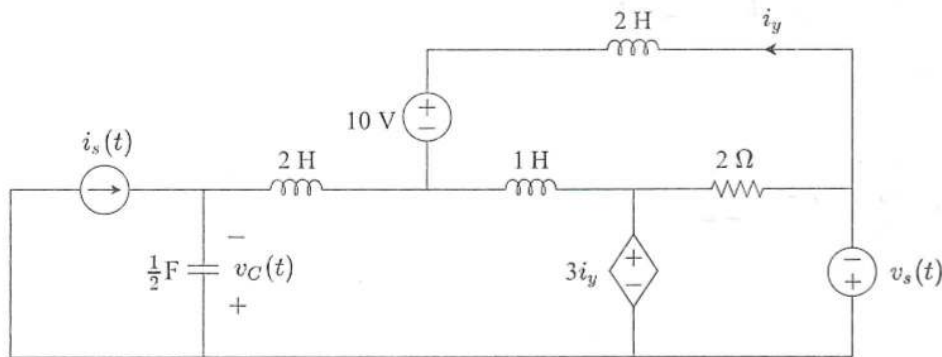2. In the circuit below, $i_s(t) = 2 \cos t$ A and $v_s(t) = 5 \sin(2t + 15^\circ)$ V. Find the capacitor voltage, $v_C(t)$.

$$v_C(t) = 10 \cos(t + 143.13^\circ) + 15.81 \cos(2t - 146.6^\circ) + 10 \text{ V}$$




must use superposition since sources are not the same ω .

only $i_s(t)$: $\omega = 1$.

$$i_s(t) = 2 \angle 0^\circ$$

nodal:

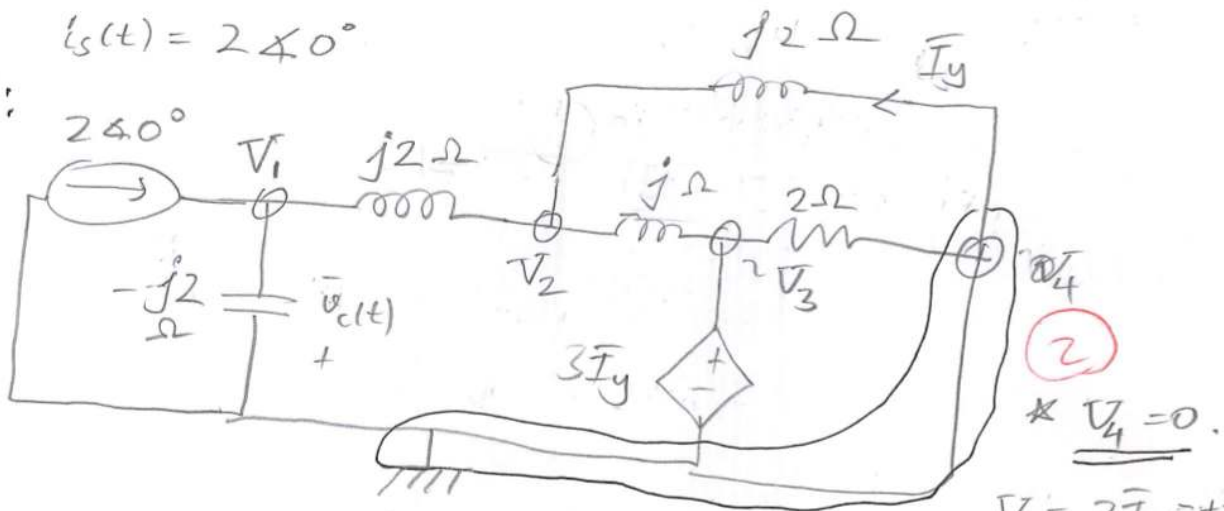

KCL ①:

$$-2 \angle 0^\circ + \frac{V_1}{-j2} + \frac{V_1 - V_2}{j2} = 0 \quad (2)$$

KCL ②:

$$\frac{V_2 - V_1}{j2} + \frac{V_2 - V_4}{j2} + \frac{V_2 - V_3}{j} = 0$$

$$-\frac{V_3}{j} = -\frac{j^3 \frac{\sqrt{2}}{2}}{j} = -\frac{3\sqrt{2}}{2}$$

$$-\frac{V_3}{j} = -\frac{3I_y}{j} = 1 \quad \frac{V_2}{j2} = +\frac{3\sqrt{2}}{2}$$

$$\Rightarrow \cancel{-240^\circ} \quad \cancel{V_1 \left(-\frac{1}{j2} + \frac{1}{j2} \right)} + V_2 \left(-\frac{1}{j2} \right) = 240^\circ \quad (1)$$

$$\Rightarrow V_1 \left(-\frac{1}{j^2} \right) + V_2 \left(\frac{1}{j^2} + \frac{1}{j^2} + \frac{1}{j} - \frac{3}{2} \right) = 0. \quad (2)$$


① \Rightarrow $V_2 = \frac{240^\circ}{-\frac{1}{j^2}} = -4j \checkmark$

$$\Rightarrow V_1 = -V_2 \left(-\frac{3}{2} - 2j\right) = 4j \left(-\frac{3}{2} - 2j\right) = 8 - j6$$

$$\therefore v_c'(t) = -v_1 = -8 + j6$$

$$= 10 \cos(t + 143.13^\circ) \text{ V}$$

Second part: only $U_3(\pm)$:

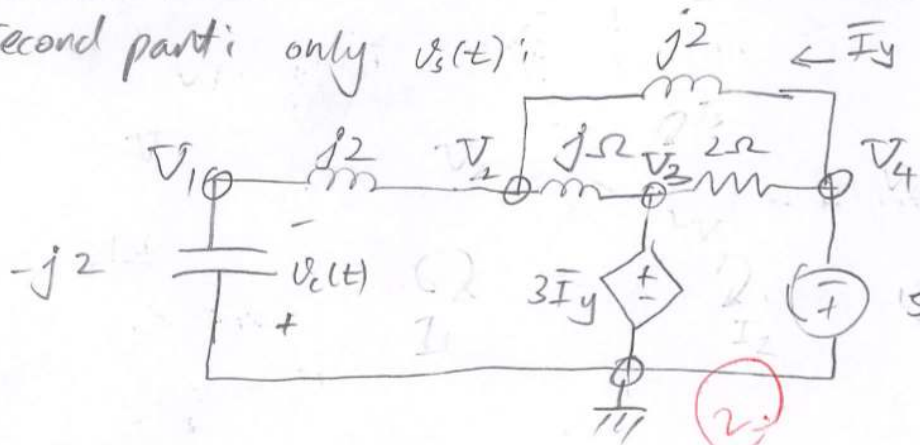

$$\underline{w = 2}$$

$$\sin(2t + 15^\circ)$$

$$= \cos(2t - 75^\circ)$$

$$\text{KCL i: } \frac{V_1}{-j2} + \frac{V_1 - V_2}{-j2} = 0$$

$$\frac{V_2 - V_4}{j2} + \frac{V_2 - V_1}{j2} + \frac{V_2 - V_3}{j} = 0$$

KL 4; $V_4 = -54.75^\circ$

KCL 3;

$$V_3 = 3 \bar{I}_y = 3 \cdot \frac{V_4 - V_2}{j2}$$

$$\Rightarrow \textcircled{1}: V_1 \left(-\frac{1}{j2} + \frac{1}{j2} \right) + V_2 \left(-\frac{1}{j2} \right) = 0$$

$$\textcircled{2}: V_1 \left(-\frac{1}{j2} \right) + V_2 \left(\frac{1}{j2} + \frac{1}{j2} + \frac{1}{j} \right) - \frac{V_3}{j} - \frac{V_4}{j2} = 0$$

$$\star \begin{cases} V_4 = -5 \angle -75^\circ \\ V_3 = \frac{3}{j2} (V_4 - V_2) \end{cases}$$

$$\Rightarrow \textcircled{1}: V_2 \cdot \frac{-1}{j2} = 0 \Rightarrow V_2 = 0.$$

$$\Rightarrow \textcircled{2}: V_1 \left(-\frac{1}{j2} \right) + \frac{3}{2} (-5 \angle -75^\circ) + \frac{5 \angle -75^\circ}{j2} = 0.$$

$$V_1 \left(-\frac{1}{j2} \right) + 1.9411 + 7.244j + -2.4148 - 0.647j = 0$$


$$V_1 \left(-\frac{1}{j2} \right) = 4.3559 - 6.597j$$

$$= -13.194 - 8.7118j$$


$$V_c(t) = -V_1 = -15.81 \angle -146.6^\circ.$$

$$= -15.81 \cos(2t - 146.6^\circ)$$

final part: just DC:

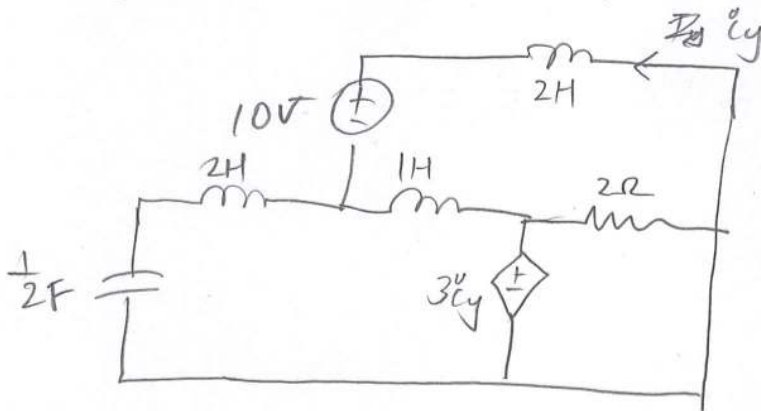

⇒ DC cond.
Short ind
open cap.

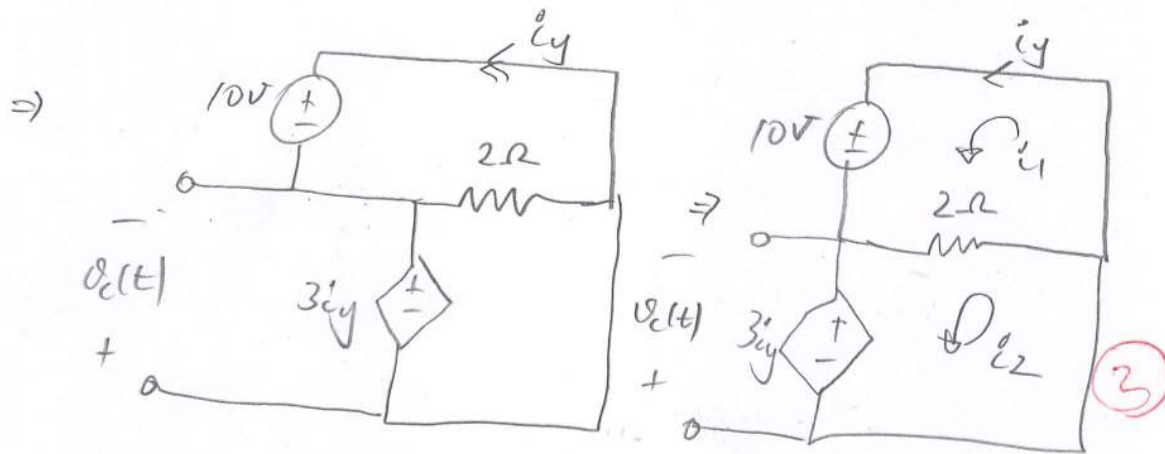

$$\begin{aligned} (1): +10 + 2(\dot{i}_1 - \dot{i}_2) &= 0 \Rightarrow 2\dot{i}_1 - 2\dot{i}_2 = -10 \\ (2): +3\dot{i}_1 + 2(\dot{i}_2 - \dot{i}_1) &= 0 \Rightarrow \dot{i}_1 + 2\dot{i}_2 = 0 \end{aligned}$$

$$\dot{i}_1 = -\frac{10}{3} \text{ A}$$

$$\dot{i}_2 = \frac{5}{3} \text{ A}$$

$$v_c(t) = -3\dot{i}_y = -3\dot{i}_1 = -3\left(-\frac{10}{3}\right) = 10 \text{ V} \quad (1)$$

All together:

$$v_c(t) = 10 - 15.81 \cos(2t - 146.6^\circ) + 10 \cos(t + 143.13^\circ)$$

Name: _____

Student No.: _____


Name: _____

3. In the circuit below, $v_s(t) = 5 \cos(1000t)$ V and $i_s(t) = 2 \sin(1000t - 30^\circ)$ mA. The circuit is in the steady state condition.

(a) Find $i_x(t)$.

(b) Find $v_y(t)$.

| | |
|---|---|
| $i_x(t) = 0.023 \cos(1000t - 93.7^\circ)$ | A |
| $v_y(t) = 22 \cos(1000t + 4.11^\circ)$ | V |

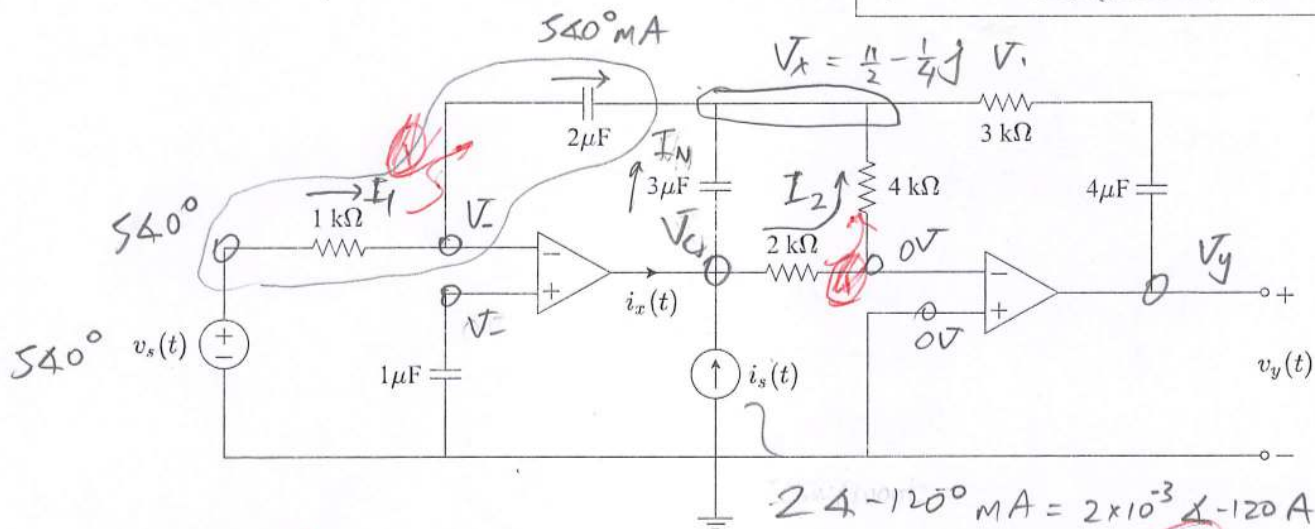

$$I_1 = \frac{540^\circ}{1k\Omega} = 5.40^\circ \text{ mA} = 5 \times 10^{-4} \angle 40^\circ \text{ A}$$

$$\frac{V_x - 540^\circ \text{ V}}{-j} = 5 \times 10^{-4} \angle 40^\circ \text{ A}$$

$$\frac{1000 \times 2 \times 10^{-6}}{1000 \times 2 \times 10^{-6}} + 1000$$

$$V_x = \frac{11}{2} - \frac{1}{4}j \text{ V}$$

$$I_2 = \frac{0 - V_x}{4000} = 1.376 \times 10^{-3} \angle 177.4^\circ \text{ A}$$

$$\frac{V_c - 0}{2000} = I_2, \quad V_c = -\frac{11}{4} + j\frac{1}{8} \text{ V}$$

$$I_N = \frac{V_c - V_x}{-j} = 0.0248 \angle -92.6^\circ \text{ A}$$

$$\frac{3 \times 1000 \times 10^{-6}}{3 \times 1000 \times 10^{-6}}$$

KCL @ centre: $2 \times 10^{-3} \angle -120^\circ + i_x(t) = 1.376 \times 10^{-3} \angle 177.4^\circ + 0.0248 \angle -92.6^\circ$

Name: [REDACTED]

$$\text{Solving: } i_x(t) = -1.5 \times 10^{-3} \angle -0.023 \\ = 0.023 \cos(1000t - 93.7^\circ)$$

$$\frac{V_y - V_x}{3000 + \frac{j}{3 \times 10^{-6} \cdot 1000}} = I_1 + I_2$$

$$\Rightarrow V_y - V_x = \frac{50000 + 6.242j}{3000 + \dots} \\ = 16.463 + 1.83j$$

$$V_y = 22 + 1.38j \\ = 22.02 \angle 4.11$$

$$v_y(t) = 22.02 \cos(1000t + 4.11^\circ)$$

Name: _____

Student No.: _____

Name: _____

Student No.: _____


Name: _____

Student No.: _____

4. In the circuit below, the frequency of the sources is 1000 rad/s.


★ Fix RMS! (a) Find the Thevenin equivalent circuit (V_{th} and Z_{th}) seen between terminals A and B.

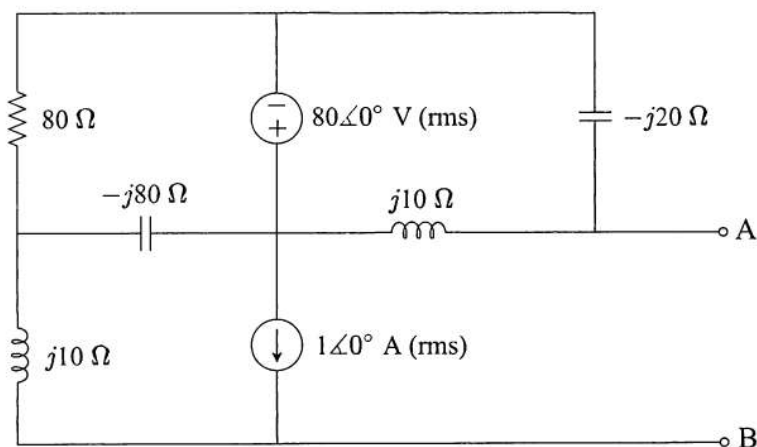(b) A load is to be connected between terminals A and B. This load is composed of a resistor, R_o , and an inductor, L_o , connected in series. R_o and L_o can be changed within $[0, 30] \Omega$ and $[5, 15] \text{ mH}$, respectively. Find the maximum average power, P_o , that can be delivered to R_o .



| |
|--|
| $V_{th} = 80 - j10 \text{ V (rms)}$ |
| $Z_{th} = 40 - j10 \Omega \text{ (rms)}$ |
| $P_o = 39.8 \text{ W}$ |

a) V_{th} :

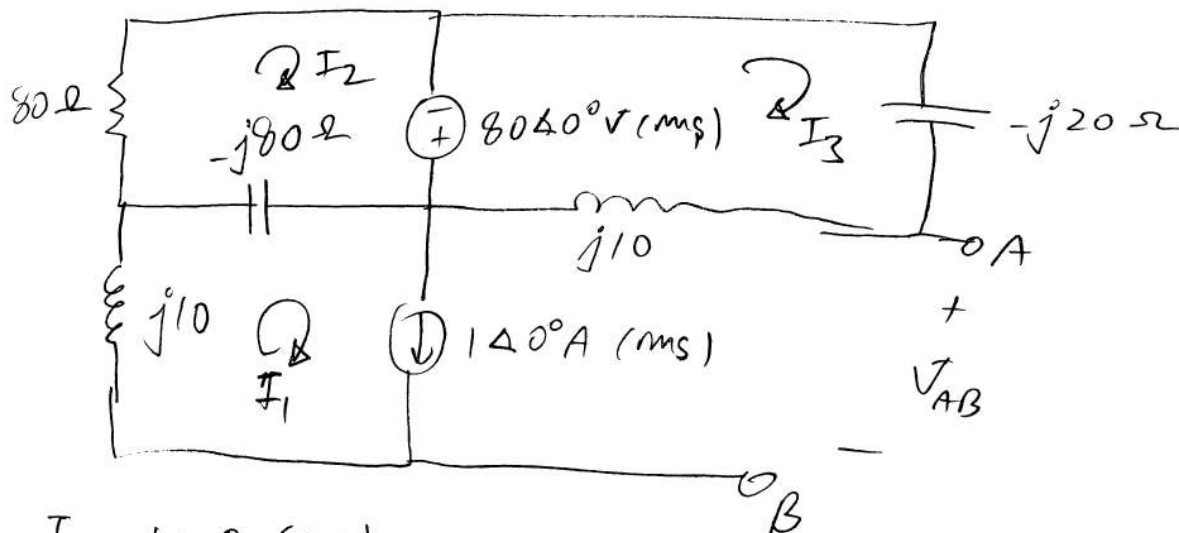

$$\underline{I_1 = 1 \angle 0^\circ \text{ (rms)}}$$

$$\text{loop 2: } I_2(80) - 80 \angle 0^\circ \text{ V (rms)} + (-j80)(I_2 - I_1) = 0$$

$$\text{loop 3: } 80 \angle 0^\circ \text{ V (rms)} + (-j20)I_3 + (j10)(I_3) = 0,$$

$$\hookrightarrow I_3 = \frac{-80 \angle 0^\circ}{j10 - j20} = \underline{\underline{-8j \text{ (rms)}}}$$

$$I_2(80) - 80 \angle 40^\circ + (-j80)(I_2 - 1 \angle 40^\circ) = 0$$


$$(80 - j80) I_2 = 80 \angle 40^\circ - (1 \angle 40^\circ)(j80)$$

$$\underline{I_2 = 1 \angle 40^\circ}$$

$$\text{KVL: } + V_{AB} + j10 I_1 + 80 I_2 - j20 I_3 = 0$$

$$V_{AB} = j20(-8j) - 80(1) - j10(1) = 80 - 10j \text{ (mV)} \quad \checkmark$$


Z_{th} : first method:

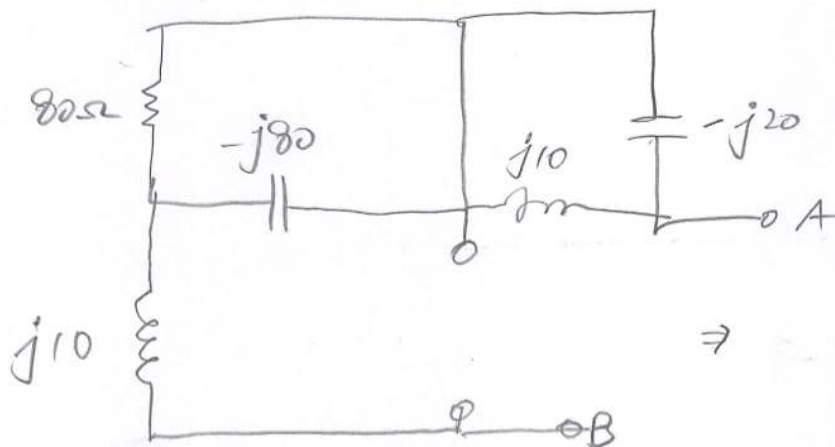

$$(80 \parallel -j80) + (j10 \parallel -j20)$$

$$\frac{(80)(-j80)}{80 - j80} + \frac{(j10)(-j20)}{j10 - j20}$$

$$= 40 - 20j$$

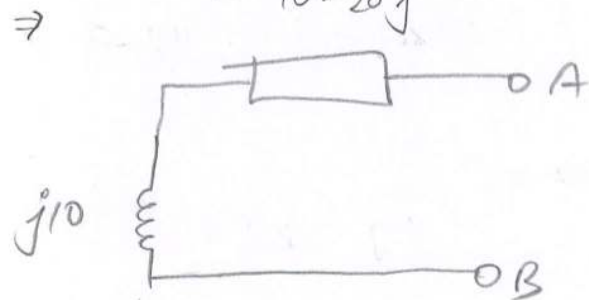


$$\Rightarrow Z_{th} = 40 - j10 \, \Omega \text{ (mV)} \quad \checkmark$$

b)

$$0 \leq R_o \leq 30 \, \Omega$$

$$5 \leq L_o \leq 75 \text{ mH}$$

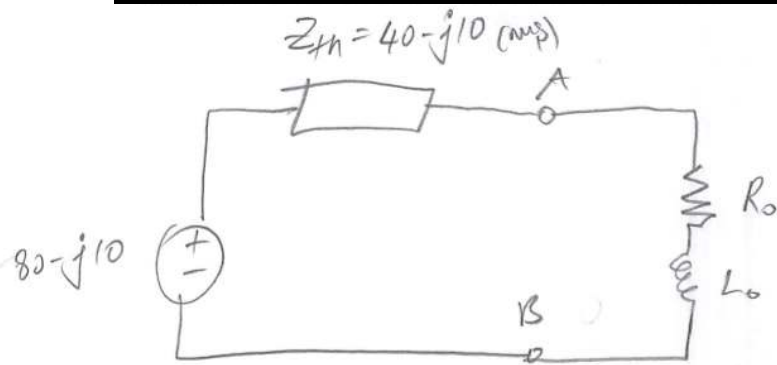

Under no restrictions:

$$Z_L = R_o + jX_L$$

$$X_L = -X_{th} = 10.$$

$$R_L = \sqrt{(40)^2 + (X_L + X_{th})^2} = 40 \Omega.$$

So, choose closest $R_o = 30 \Omega$ ✓

For L_o :

$$5 \times 10^{-3} < L_o < 15 \times 10^{-3} \text{ H}$$

$$\omega = 1000 \text{ rad/s}$$

$$5 < \omega L_o < 15$$

$5 < X_L < 15 \rightarrow$ want ideal case of 10 \rightarrow possible!

$$\therefore Z_L = 30 + j10 \Omega \text{ ✓}$$

Max power:

$$P_{avg} = \frac{1}{2} R_L |\bar{I}|^2$$

$$\text{KVL: } 80 - j10 + j10 \bar{I} + 30 \bar{I} + \bar{I}(40 - j10) = 0$$

$$\bar{I} = \frac{j10 - 80}{j10 + 30 + 40 - j10} = -\frac{8}{7} + \frac{1}{7}j \text{ (mp)}$$

$$P_{avg} = \frac{1}{2} (30) \left(\frac{\sqrt{65}}{7} \right)^2 = 19.898 \text{ W}$$

$$\Rightarrow P_{avg} = 2 \cdot 19.898 = 39.8 \text{ W} \text{ ✓}$$

Name: _____

Student No.: _____


Name: _____

Student No.: _____

5. In the circuit below, the voltage at the terminal of the loads is $120\angle 0^\circ$ V (rms). Find

- (a) the source voltage, V_s ,
 (b) the current drawn from the source, I_s , and
 (c) the total complex power delivered by the source, S_s .

| |
|-----------------------------------|
| $V_s = 174.9 \angle 0.2914^\circ$ |
| $I_s = 5.204 \angle -1.66^\circ$ |
| $S_s = 624.16 + j18.14$ |

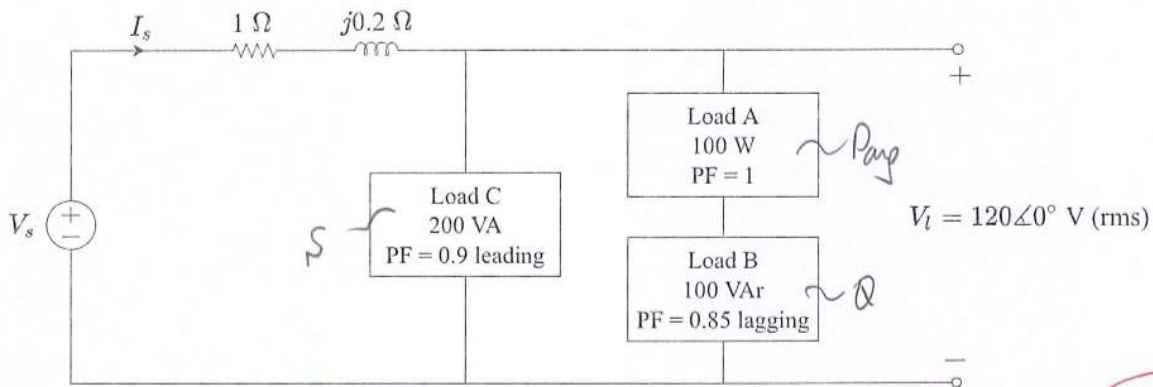

b)

A: $P_{avg} = 100 \text{ W} = S \cdot PF$. $\therefore S = 100 \text{ W} \Rightarrow \bar{S} = 100 \angle 0^\circ \rightarrow$ since $PF = 1$.

B: $Q = 100 \text{ VAR} = S \sin \theta$, $\theta = \cos^{-1}(0.85) = \pm 31.79^\circ \rightarrow \text{lag} \rightarrow \theta = 31.79^\circ$.
 $\Rightarrow S = \frac{100}{\sin \theta} = 189.82 \text{ VA} \Rightarrow \bar{S} = 189.82 \angle 31.79^\circ$.

C: $S = 200 \text{ VA} \rightarrow \theta = \cos^{-1}(0.9) = -25.842^\circ (\text{lead}) \Rightarrow \bar{S} = 200 \angle -25.84^\circ$.

$\bar{S}_{tot} = 100 \angle 0^\circ + 189.82 \angle 31.79^\circ + 200 \angle -25.84^\circ = 441.347 + j12.83$.

$S_{tot} = V_l I_s^*$, $I_s = \frac{S_{tot}^*}{V_l^*} = \frac{441.347 - j12.83}{120 \angle 0^\circ} = 3.68 \angle -1.66^\circ \text{ A}$.

$\therefore I_s = \sqrt{2} I_{rms} = 5.204 \angle -1.66^\circ$

a) KVL:

$V_l + I_s(1) + I_s(j0.2) = V_s = \sqrt{2} 120 \angle 0^\circ + (1 + j0.2) I_s$
 $= 174.9 \angle 0.2914^\circ$.

$S_s ?$

Name: _____

Student No.: _____

Name: _____

Student No.: _____

Name: _____

Student No.: _____

Name: _____

Student No.: _____

Name: _____

Student No.: _____

Name: _____

Student No.: _____