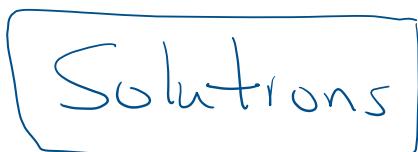


# ECE159H1: Fundamentals of Electric Circuits

*Midterm – Tuesday March 5, 2024  
9 AM – 10:50 AM*




- Make sure to **accurately** enter your first name, last name, and student number above.
- The Midterm is worth 80 marks and has four questions. Each question is worth 20 marks.
- Show all of your work, and the final page is left blank which you can use for rough work or for extra space for your answers.
- Marks are allocated for neatness and clarity of communication in your answers.
- Take a deep breath, relax, and enjoy 😊.

### Question #1 (20 marks)

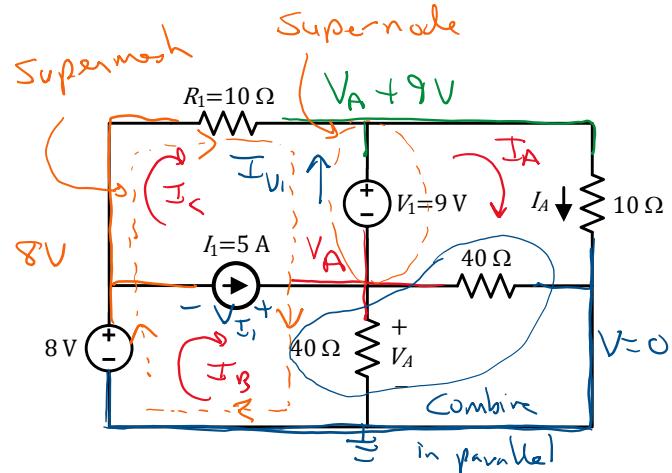1. Consider the circuit shown to the right. Use nodal or mesh analysis to find the powers of the sources  $V_1$  and  $I_1$ , and the power of the resistor  $R_1$ . If you want, you can make any reasonable simplifications before you apply nodal or mesh analysis.

- (5 marks) (a) Take a few minutes to consider how you plan to analyze this circuit to determine the quantities you are asked to find.



Briefly describe your proposed plan below. Your plan should be specific in terms of

- Any simplifications you plan to make before your analysis,
- How you plan to set up your nodal or mesh analysis to solve the circuit (i.e., where is the ground node, how are your mesh currents defined, do you need to use any supernodes or supermeshes?), and
- How you plan to use the results of your analysis to calculate the quantities you need to find.

This should be mostly in words, with some equations as needed. Make sure you clearly label all of the unknown quantities you plan to use on the circuit above. The use of bullet points is preferred.

### Possible Answers

#### Nodal Analysis

- Combine  $40\Omega \parallel 40\Omega$  between node A & ground
- Putting the ground at bottom node results in one unknown,  $V_A$
- Plan: → Do KCL @ supernode to find  $V_A$   
→ Once  $V_A$  is known, find  $I_{V1}$  from KCL @ node A.  
→ Once  $V_A$  &  $I_{V1}$  are known:

$$P_{R1} = \frac{[8 - (V_A + 9)]^2}{10}, P_{I1} = 5(8 - V_A)^2$$

$$P_{V1} = I_{V1} V_1 = I_{V1} (9)$$

#### Mesh Analysis


- Combine  $40\Omega \parallel 40\Omega$  to eliminate one of the meshes
- Define mesh currents as shown on the circuit → three unknowns
- Plan: → Do KVL for supermesh, and mesh A to solve for three unknowns  
→ Do KVL in mesh B to find  $V_{I1}$   
→ Once all currents and  $V_{I1}$  are known:  
 $P_{R1} = I_c^2 R_1 = 10 I_c^2$   
 $P_{I1} = I_{V1} V_{I1}, P_{V1} = V_1 (I_A - I_c)$

### Question #1 (continued)

- (9 marks) 1. (b) Follow through with the first two steps of the plan you developed in part (a), by making any appropriate simplifications (if necessary), and then completing nodal or mesh analysis.

If you do nodal analysis, enter your answer for  $V_A$  in the box below. If you do mesh analysis, enter your answer for  $I_A$  in the box below.

Redrawing:

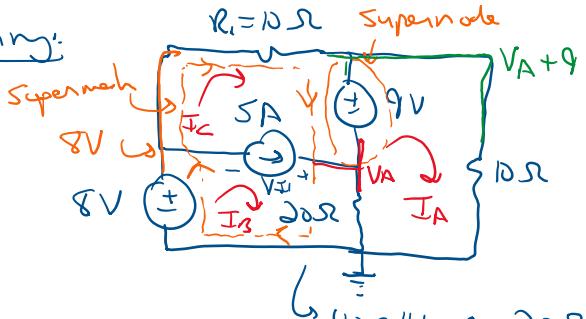

Nodal Analysis

KCL @ Supernode:

$$40(5) = \left( \frac{V_A}{40} + \frac{V_A}{40} + \frac{(V_A+9)-8}{10} + \frac{V_A+9}{10} \right) 40$$

$$V_A + V_A + 4V_A + 36 - 32 + 4V_A + 36 = 200$$

$$V_A = \frac{160}{10} = 16V$$

KCL @ A:

$$\begin{aligned} I_{V_1} &= 5 - \frac{V_A}{40} - \frac{V_A}{40} \\ &= 5 - \frac{16}{40} - \frac{16}{40} = 4.2A \end{aligned}$$

Mesh Analysis

KVL for mesh A:

$$10I_A + 20(I_A - I_B) = 9$$

$$30I_A - 20I_B = 9 \quad (1)$$

KVL for Supermesh:

$$20(I_B - I_A) - 8 + 10I_C + 9 = 0$$

$$-20I_A + 20I_B + 10I_C = -1 \quad (2)$$

Constraint Eq:  $I_B - I_C = 5 \quad (3)$

Solving system of three equations

$$I_A = 2.5A, I_B = 3.3A, I_C = -1.7A$$

KVL for Mesh B:

$$8 + V_{\pm 1} = 20(I_B - I_A) \rightarrow V_{\pm 1} = 8V$$

For those who did nodal analysis:

$$V_A = \underline{\hspace{2cm}} 16V \underline{\hspace{2cm}}$$

For those who did mesh analysis:

$$I_A = \underline{\hspace{2cm}} 2.5A \underline{\hspace{2cm}}$$

**Question #1 (continued)**

- (6 marks) 1. (c) Determine the quantities you were asked to find at the beginning of this question. Enter your final answers in the boxes below. Use the standard convention that a negative value for power indicates supplied power.

Using equations from part (a) :

Nodal

$$P_{R1} = \frac{[8 - (V_A + 9)]^2}{10}$$

$$= \frac{[8 - (16 + 9)]^2}{10} = \underline{\underline{28.9 \text{ W}}}$$

Mesh

$$P_{R1} = I_C^2 R_1 = 10 I_C^2 = 10(-1.7)^2 = \underline{\underline{28.9 \text{ W}}}$$

$$P_{I_1} = I_{V_1} V_{I_1} = (5)(8) = \underline{\underline{40 \text{ W}}} \text{ (Supplying)}$$

$$P_{I_1} = 5(8 - V_A)^2$$

$$= 5(8 - 16)^2 = \underline{\underline{40 \text{ W}}}$$

(Supplying)

$$P_{V_1} = V_1 (I_A - I_C) = (9)[2.5 - (-1.7)]$$

$$= \underline{\underline{37.8 \text{ W}}} \text{ (Supplying)}$$

$$P_{V_1} = 9 I_{V_1} = 9(4.2)$$

$$= \underline{\underline{37.8 \text{ W}}}$$

(Supplying)

Power of the source  $I_1$

$$P_{I_1} = \underline{\underline{-40 \text{ W}}}$$

Power of the source  $V_1$

$$P_{V_1} = \underline{\underline{-37.8 \text{ W}}}$$

Power of the resistor  $R_1$


$$P_{R1} = \underline{\underline{+28.9 \text{ W}}}$$

### Question #2 (20 marks)

- (8 marks) 2. (a) In the circuit shown to the right, it is known that  $I_0 = -2 \text{ A}$  and  $I_1 = \frac{23}{73} \text{ A}$ .

Use this information to determine the current  $I_2$ , the voltage  $V_1$ , and the powers supplied by the 3 A source and the dependent source. Enter your answers in the boxes below.

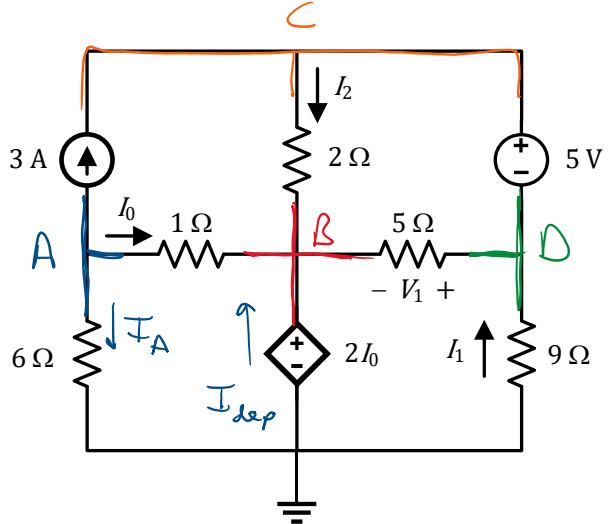Note: You do not need to apply nodal or mesh analysis to solve this problem. But make sure to clearly justify your answers based on fundamental circuit analysis principles.



$$1) \text{ From KCL at } A: I_A + 3 + I_0 = 0 \rightarrow I_A = -3 - (-2) = -1 \text{ A}$$

$$\therefore V_A = 6(I_A) = -6 \text{ V}$$

$$2) \text{ Observe } V_B = 2I_0 = 2(-2) = -4 \text{ V}$$

$$3) \text{ Observe } V_D = -9I_1 = -9\left(\frac{23}{73}\right) = -\frac{207}{73} = -2.84 \text{ V}$$

$$4) \text{ Observe } V_C = 5 + V_D = \frac{158}{73} \approx 2.16 \text{ V}$$

$$5) \text{ KCL at } B \text{ gives: } I_0 + I_{dep} + \frac{V_C - V_B}{2} + \frac{V_D - V_B}{5} = 0 \rightarrow I_{dep} = -\frac{96}{73} = -1.315 \text{ A}$$

$$\therefore I_2 = \frac{V_C - V_B}{2} = \frac{\frac{158}{73} - (-4)}{2} = \frac{225}{73} \approx 3.08 \text{ A}$$

$$V_1 = V_D - V_B = -\frac{207}{73} - (-4) = \frac{85}{73} \approx 1.16 \text{ V}$$

(Supplying)

$$P_{3A} = 3(V_C - V_A) = 24.5 \text{ W} \quad (\text{Supplying}), \quad P_{dep} = (2I_0)I_{dep} = \frac{384}{73} \approx 5.26 \text{ W}$$

Current $I_2$
---------------

$$I_2 = \frac{225}{73} = 3.08 \text{ A}$$

Voltage $V_2$
---------------

$$V_2 = \frac{85}{73} \approx 1.16 \text{ V}$$

Power of 3 A Source
---------------------

$$P_{3A} = -24.5 \text{ W}$$


Power of Dependent Source
---------------------------

$$P_{dep} = -5.26 \text{ W}$$
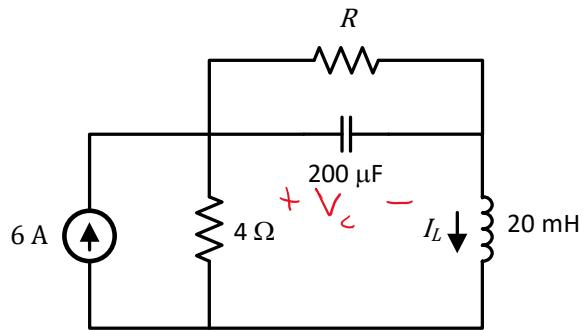
### Question #2 (continued)


- (6 marks) 2. (b) The circuit to the right has been in this state for a long time, meaning the circuit has reached its steady-state condition.

Determine if each of the following statements are **True** or **False**, and circle your answer. Provide a brief justification for your answer in words or with appropriate calculations for each choice.



True     False

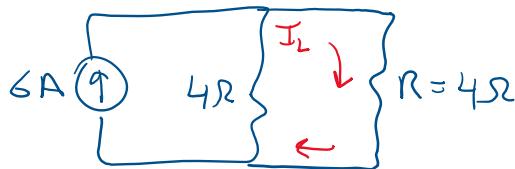- (i) If  $R = 4 \Omega$ , then the current through the inductor is  $I_L = 3 \text{ A}$ .  
At steady-state:



$$I_L = 6 \left( \frac{V_L}{V_L + V_R} \right) = \underline{\underline{3 \text{ A}}}$$

True


True     False

- (ii) A resistance of  $R = 10 \Omega$ , would ensure that the energy stored in the capacitor is equal to the energy stored in the inductor.

At steady state:

$$V_C = 6(4/10) = 6(2.857\Omega) = 17.143 \text{ V}$$
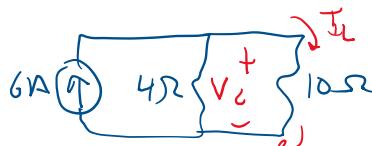
$$I_L = 6 \left( \frac{4}{9+10} \right) = 1.714 \text{ A}$$



$$W_C = \frac{1}{2} C V_C^2 = \frac{1}{2} (200 \times 10^{-6})(17.143)^2 = \underline{\underline{29.4 \text{ mJ}}}$$

$$W_L = \frac{1}{2} L I_L^2 = \frac{1}{2} (20 \times 10^{-3})(1.714)^2 = \underline{\underline{29.4 \text{ mJ}}}$$

$\therefore$  With  $R = 10 \Omega$ ,  $W_C = W_L \rightarrow \underline{\underline{\text{True}}}$

True     False

- (iii) The  $200 \mu\text{F}$  capacitor is a parallel-plate capacitor. To double the value of the capacitance, one should double the spacing between the parallel plates.


$C = \frac{\epsilon A}{d} \rightarrow$  To double  $C$ , one must halve  $d$ .

$\hookrightarrow \underline{\underline{\text{False}}}$

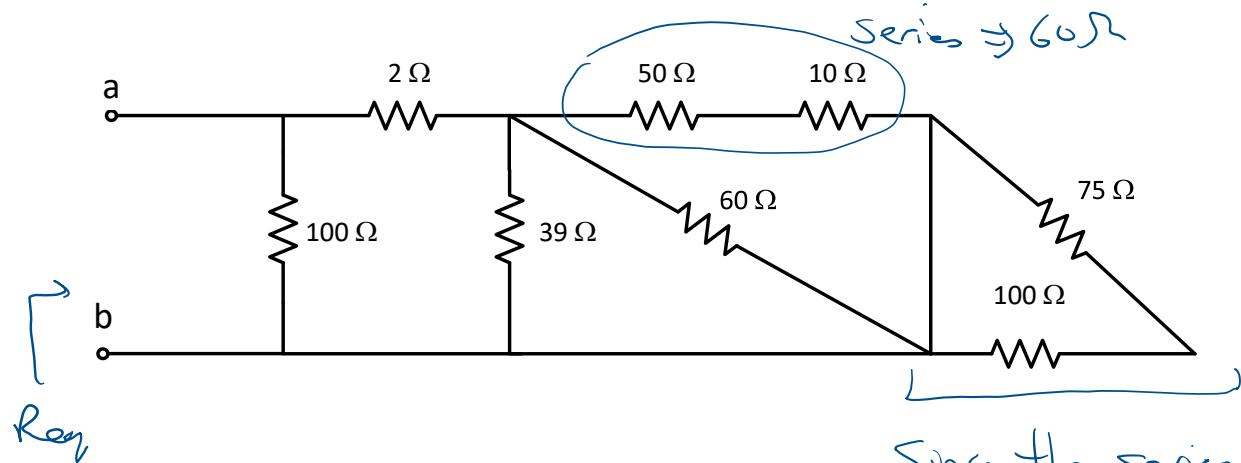**Question #2 (continued)**


(6 marks) 2. (c) Find the equivalent resistance as seen from terminals a-b for the circuit shown below.

Be sure to provide a clear description of your steps to find the equivalent resistance.  
Enter your answer (to one decimal place) in the box below.



Since the series combination of the 100Ω and 75Ω resistor is shorted out, they don't contribute to  $R_{eq}$ .

Redrawing

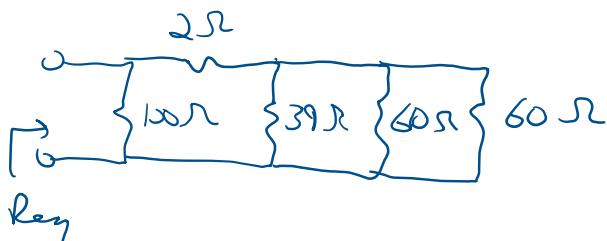

$$\therefore R_{eq} = 100 \parallel (2 + 39 \parallel 60 \parallel 60)$$

$$= \left[ \frac{1}{100} + \frac{1}{2 + \left[ \frac{1}{39} + \frac{1}{60} + \frac{1}{60} \right]^{-1}} \right]$$

$$= \left[ \frac{1}{100} + \frac{1}{2 + 16.9565} \right]$$


$$= 15.9 \Omega$$

Equivalent Resistance

$$R_{eq} = \underline{\underline{15.9 \Omega}}$$

**Question #3 (20 marks)**

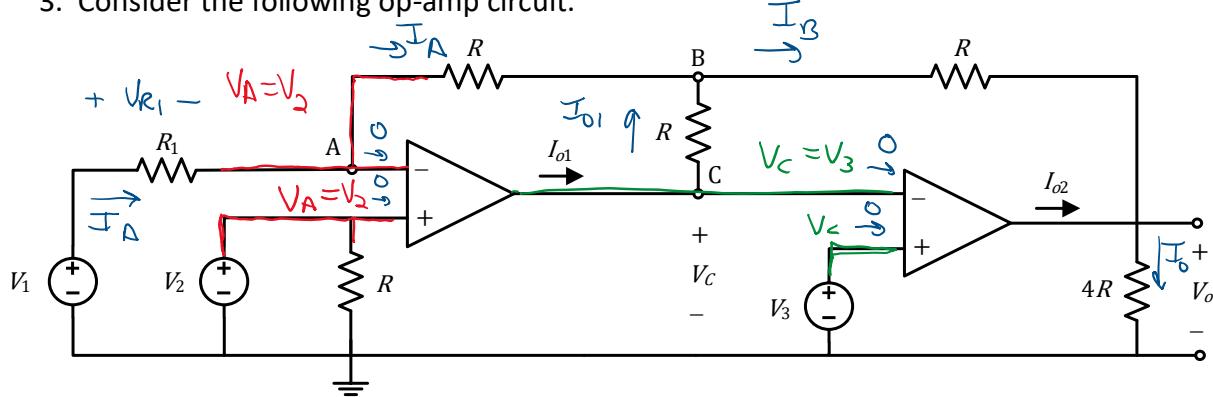3. Consider the following op-amp circuit.



- (6 marks) (a) Apply the ideal op-amp model to this circuit, and describe three conclusions about the operation of the circuit you can make as a result of using this ideal model. For example, consider what this model tells you about the voltages  $V_A$  and  $V_C$ . You do not need to do any calculations for this part, and your answer can be in words or simple equations.

Possible Answers (should have 3)

- Observe  $V_A = V_2$
- Observe  $V_C = V_3$
- Observe  $I_A = \frac{V_{R1}}{R_1} = \frac{V_1 - V_A}{R_1} = \frac{V_1 - V_2}{R_1}$
- Observe the current through  $R_1$ ,  $I_A$ , is the same as that through the first feedback resistor,  $R$
- The above point means:  $I_A = \frac{V_1 - V_2}{R_1} = \frac{V_2 - V_B}{R} \rightarrow V_B = V_2 - \frac{R}{R_1}(V_1 - V_2) = \left(1 + \frac{R}{R_1}\right)V_2 - \frac{R}{R_1}V_1$
- Observe  $I_B = I_A + I_{o1}$
- Observe  $I_{o1} = \frac{V_C - V_B}{R} = \frac{V_3 - V_B}{R} = \frac{V_3}{R} + \frac{V_1}{R_1} - \left(\frac{1}{R} + \frac{1}{R_1}\right)V_2$

**Question #3 (continued)**

(10 marks) (b) Determine the expression for the output voltage  $V_0$  in terms of  $V_1, V_2, V_3, R_1$  and  $R$ .

Applying KCL @ B:  $I_B = I_A + I_{o1}$

But  $I_B = \frac{V_B - V_o}{R}$  and using  $V_B = \left(1 + \frac{R}{R_1}\right)V_2 - \frac{R}{R_1}V_1$

$$I_A = \frac{V_1 - V_2}{R_1}$$

$$I_{o1} = \frac{V_3}{R} + \frac{V_1}{R_1} - \left(\frac{1}{R} + \frac{1}{R_1}\right)V_2$$

from  
above

$$\left(\frac{1}{R} + \frac{1}{R_1}\right)V_2 - \frac{1}{R_1}V_1 - \frac{V_3}{R} = \frac{V_1}{R_1} - \frac{V_2}{R_1} + \frac{V_3}{R} + \frac{V_1}{R_1} - \left(\frac{1}{R} + \frac{1}{R_1}\right)V_2$$

$$\therefore V_o = R \left[ 2\left(\frac{1}{R} + \frac{1}{R_1}\right)V_2 + \frac{V_2}{R_1} - \frac{V_3}{R} - \frac{3V_1}{R_1} \right]$$

$$= -\frac{3R}{R_1}V_1 + \left(2 + 3\frac{R}{R_1}\right)V_2 - V_3$$

**Question #3 (continued)**

(4 marks)

- (c) Given the values of  $V_1 = 4\text{ V}$ ,  $V_2 = 2\text{ V}$ ,  $V_3 = 1\text{ V}$ ,  $R_1 = 2\text{ k}\Omega$  and  $R = 1\text{ k}\Omega$ , determine the op-amp output currents  $I_{o1}$  and  $I_{o2}$ . Enter your results in the boxes below.

For these values:  $V_o = \frac{-3R}{R_1}V_1 + \left(2 + \frac{3R}{R_1}\right)V_2 - V_3 = 0\text{ V}$

$$I_A = \frac{V_1 - V_2}{R_1} = 1\text{ mA}$$

$$V_B = \left(1 + \frac{R}{R_1}\right)V_2 - \frac{R}{R_1}V_1 = 1\text{ V}$$

$$I_B = \frac{V_B - V_o}{R} = 1\text{ mA}$$

$$\therefore I_{o1} = I_B - I_A = \underline{\underline{0\text{ mA}}}$$

$$I_{o2} = I_o - I_B = \frac{V_o}{4R} - I_B = \underline{\underline{-1\text{ mA}}}$$

Output current for op-amp #1:


$$I_{o1} = \underline{\underline{0\text{ mA}}}$$

Output current for op-amp #2:


$$I_{o2} = \underline{\underline{-1\text{ mA}}}$$

**Question #4 (20 marks)**

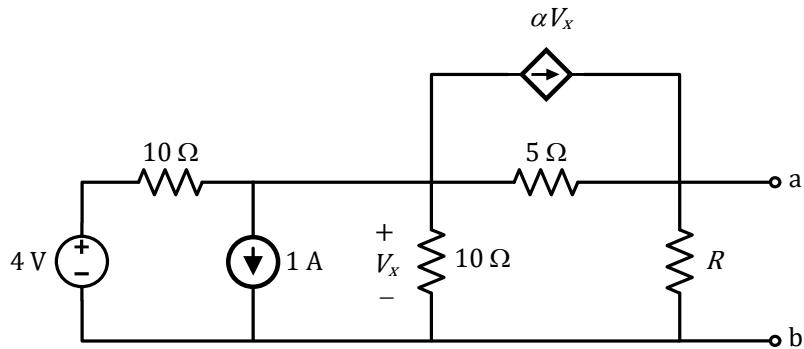4. In the circuit given below,  
 (12 marks) (a) Find the Thévenin equivalent circuit for the complete circuit, as seen at the terminals a-b.
- Enter your final answers for  $V_{Th}$  and  $R_{Th}$  in the boxes on the next page. Your answers should be in terms of  $R$  and  $\alpha$ . You may assume that  $\alpha$  is a positive constant.



To find  $V_{Th} = V_{oc}$ :

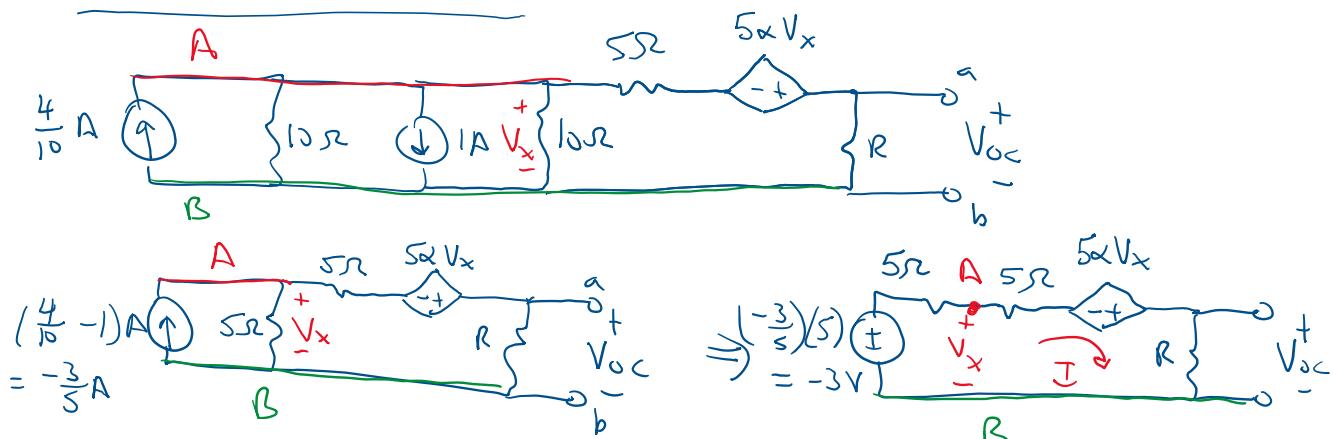

$$\text{KVL: } -3 = 5I + 5I - 5\alpha V_x + RI \quad (1)$$

$$\text{But } V_x = -5I - 3 \quad (2)$$

$$(2) \rightarrow (1) \quad -3 = (10 + R)I - 5\alpha(-5I - 3) = (10 + R + 25\alpha)I + 15\alpha$$


$$\therefore I = \frac{-3 - 15\alpha}{10 + R + 25\alpha} \rightarrow V_{oc} = V_{Th} = RI = \frac{-3(1 + 5\alpha)R}{10 + R + 25\alpha}$$

**Question #4 (continued)**

4. (a) (continued)

For  $R_{Th}$ , find  $I_{Sc}$ :

Using the above simplified circuit

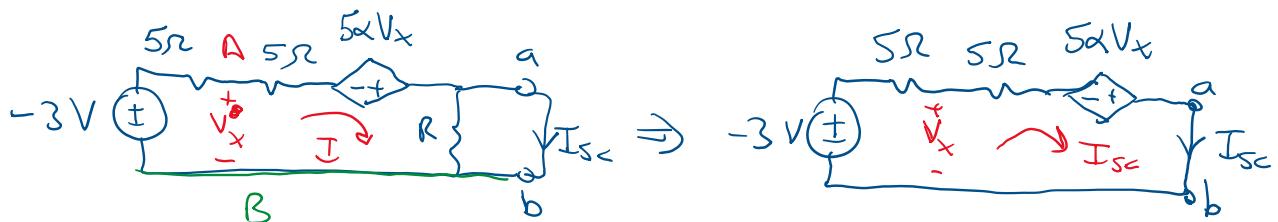

$$\therefore \text{KVL:} \quad -3 = (5 + 5)I_{Sc} - 5\alpha V_x \quad \text{but } V_x = -5I_{Sc} - 3$$

$$-3 = 10I_{Sc} - 5\alpha(-5I_{Sc} - 3)$$

$$I_{Sc} = \frac{-3 - 15\alpha}{10 + 25\alpha}$$

$$\therefore R_{Th} = \frac{V_{oc}}{I_{Sc}} = \frac{\frac{-3(1+5\alpha)R}{10+R+25\alpha}}{\frac{-3(1+5\alpha)}{10+25\alpha}} = \frac{R(10+25\alpha)}{10+25\alpha+R}$$

$$= \frac{R}{1 + \frac{R}{10+25\alpha}}$$

Thévenin equivalent source

$$V_{Th} = \frac{-3(1+5\alpha)R}{10+R+25\alpha}$$


Thévenin equivalent resistance

$$R_{Th} = \frac{R}{1 + \frac{R}{10+25\alpha}}$$

**Question #4 (cont'd)**

- (8 marks) 4. (b) Determine the required values of  $R$  and  $\alpha$  so that a maximum power of  $P_{max} = 4.39 \text{ W}$  is delivered by the circuit to a  $50 \Omega$  load resistor (i.e., a resistor that is placed across the terminals a-b).

For maximum power:

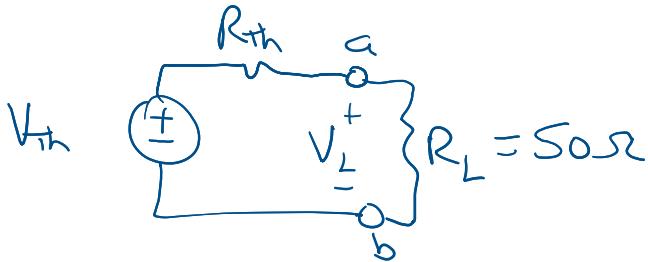

For maximum power:

$$R_{Th} = R_L = 50 \Omega$$

$$V_L = \frac{V_{Th}}{2}$$

$$\text{For } P_{max} = 4.39 \text{ W} = \frac{V_L^2}{4R_{Th}} = \frac{V_{Th}^2}{4(50)} \rightarrow V_{Th} = \pm 29.63 \text{ V}$$

$$\therefore R_{Th} = \frac{R}{1 + \frac{R}{10+25\alpha}} = 50 \rightarrow R = 50 + \frac{50R}{10+25\alpha}$$

$$\therefore 10R + 25R\alpha = 500 + 1250\alpha + 50R \rightarrow 40R + (1250 - 25R)\alpha = -500$$

$$\therefore \alpha = \frac{-500 - 40R}{1250 - 25R} = \frac{-100 - 8R}{250 - 5R}$$

Observing that  $\alpha + R$  is positive and that  $V_{Th} = \frac{-3(1+5\alpha)R}{10+R+25\alpha}$

$$\text{we choose } V_{Th} = -29.63 \text{ V} = \frac{-3(1+5\alpha)R}{10+R+25\alpha}$$

$$-29.63 - 29.63R - 740.8\alpha = -3R - 15\alpha R$$

$$-29.63 - 29.63R - 740.8 \left( \frac{-100 - 8R}{250 - 5R} \right) + 15R \left( \frac{-100 - 8R}{250 - 5R} \right) = 0$$

$$-74078 + 1481.6R - 6657.8R + 133.2R^2 + 74078 + 5926.2R - 1500R - 120R^2 = 0$$

$$13.2R^2 - 750R = 0 \rightarrow R = 0 \text{ (not relevant)} \quad R = 57 \Omega \quad \alpha = 15.9$$

Required value for  $R$ :

$$R = \underline{\underline{57 \Omega}}$$

Required value for  $\alpha$ :

$$\alpha = \underline{\underline{15.9}}$$

**This page is left intentionally blank. It can be used for rough work or extra space for your answers if you clearly direct the markers to this page.**