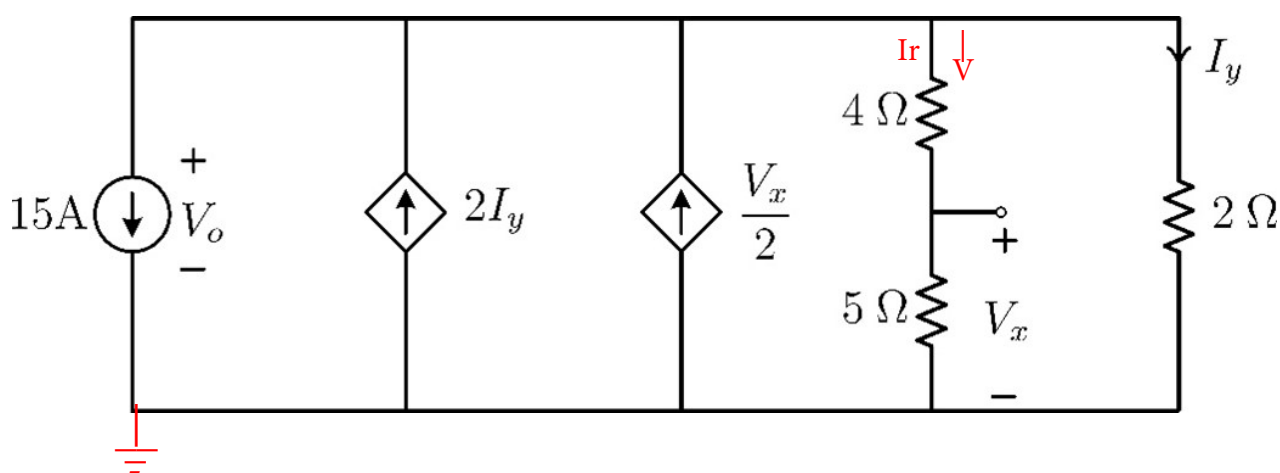


1.

Find V_o in the circuit below. Use only KCL, KVL, and Ohm's law (you will not get the mark for this question if you use other circuit analysis techniques, such as nodal analysis, mesh analysis, etc.). [5 points for correct answer, 20 points for process work]

$$V_o = \boxed{22.50 \pm 3\%} \text{ V}$$

 V_o KCL @ V_o

set current out as positive

$$(1) \quad 15 - 2I_y - 0.5V_x + I_r + I_y = 0$$

Ohm's Law for I_r , I_y

$$(2) \quad I_r = V_o / (4\Omega + 5\Omega)$$

$$(3) \quad I_y = V_o / (2\Omega)$$

Voltage division for V_x (KCL + Ohm's law)

$$(4) \quad V_x = V_o * (5\Omega / (4\Omega + 5\Omega))$$

Substitute (2),(3),(4) into (1) and solve

$$15 - 2(V_o/2\Omega) - 0.5(V_o * (5\Omega / (4\Omega + 5\Omega))) + V_o / (4\Omega + 5\Omega) + V_o / (2\Omega) = 0$$

$$270 - 18V_o - 5V_o + 2V_o + 9V_o = 0$$

$$V_o = 22.5V$$