

UNIVERSITY OF TORONTO
FACULTY OF APPLIED SCIENCE AND ENGINEERING

FINAL EXAM
April 24, 2017
2 Hours 30 Minutes

First Year – Engineering Science

ECE 159S - ELECTRIC CIRCUIT FUNDAMENTALS

Exam Type: A

Examiners: K. Phang and N.P. Kherani

NAME: _____
Last First

STUDENT #: _____

INSTRUCTIONS:


- You may write in pencil.
- This is a Type A examination; no aids are allowed.
- Only non-programmable calculators are allowed.
- The marks for each question are indicated within brackets [].
- When answering the questions, include all the steps of your work on these pages. Place your final answers in the boxes where given and include units.
- For additional space, you may use the back of the preceding page and the blank page provided at the end. Do not unstaple this exam booklet.

| | |
|--------------|------------|
| Q1 | /20 |
| Q2 | /10 |
| Q3 | /5 |
| Q4 | /10 |
| Q5 | /5 |
| Q6 | /10 |
| Q7 | /10 |
| Total | /70 |

QUESTION 1 [20 marks]



Answer the following short-answer questions.

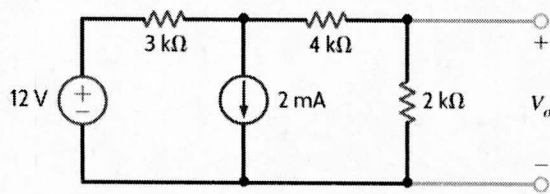- a) [2 marks] Using superposition, find V_o in the circuit shown below.




$V_o =$

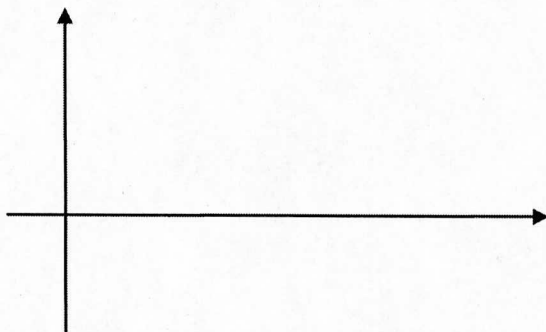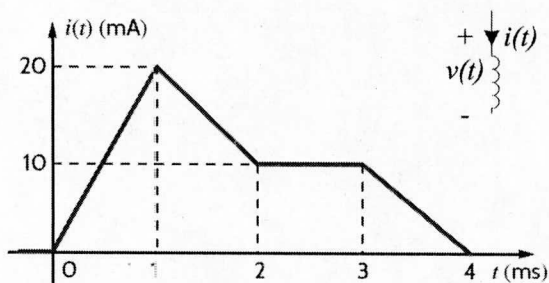- b) [2 marks] The current in a 5-mH inductor has the waveform shown below. Compute and plot the waveform for the inductor voltage. Label the axes clearly.




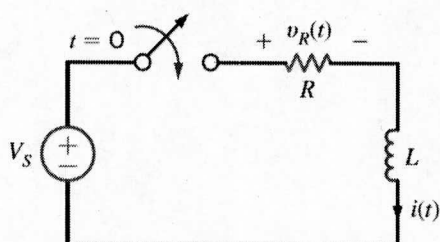- c) [1 mark] Write the differential equation for the following circuit for $t > 0$. Note, the switch is closed at $t=0$.



Question 1 (cont.)

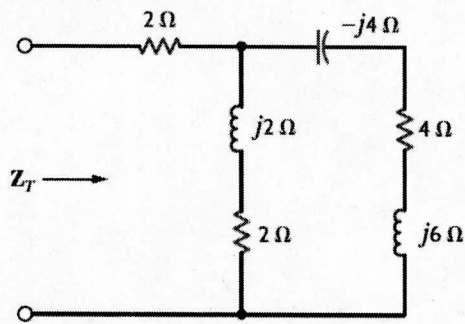d) [2 marks] Compute the impedance Z_T in the network shown below.



$Z_T =$


e) [4 marks] The complex power delivered to a load Z is $S = 100 + j57.7$ VA. If the **magnitude** of the load, $|Z| = 10\Omega$, and the angular frequency, $\omega = 377$ rad/s, calculate the equivalent series resistance, R , and inductance, L (or capacitance, C) to model the load.

$R =$

L or $C =$
(circle)


Question 1 (cont.)

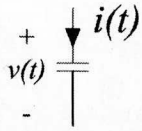- f) [2 marks] The voltage $v(t) = 100 \cos(314t + 15^\circ)$ V is applied to a $100\mu\text{F}$ capacitor. Find $i(t)$.




$i(t) =$

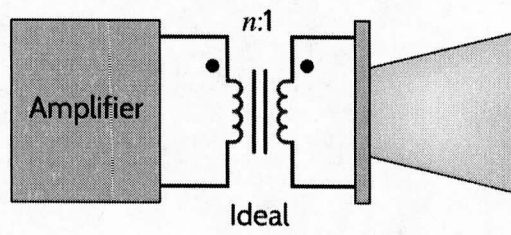- g) [2 marks] For an amplifier with an output resistance of $1.6\text{k}\Omega$, what is the turns ratio, n , of the ideal transformer required to match the amplifier to an 8Ω speaker?



$n =$

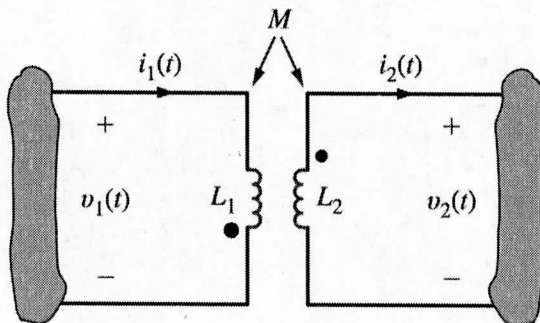
- h) [2 marks] Write the equations for voltages $v_1(t)$ and $v_2(t)$ in terms of currents $i_1(t)$ and $i_2(t)$ as shown.



Question 1 (cont.)

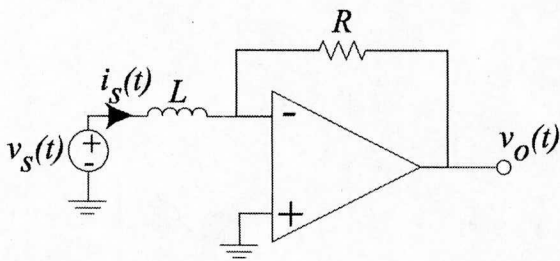i) [1 mark] What is the peak magnitude of a sinusoidal current having an rms value of 15A?


j) [2 marks] For the opamp circuit below, write an expression for the inductor current $i_s(t)$ and output voltage $v_o(t)$ in terms of the input signal, $v_s(t)$, for time $t > 0$? Assume zero initial conditions.



| |
|------------------------------|
| $i_s(t) =$ $v_o(t) =$ |
|------------------------------|

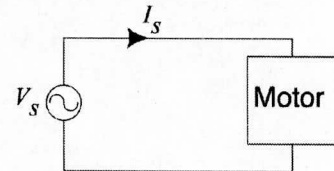QUESTION 2 [10 marks]


A 500W electric motor is connected to a sinusoidal source of 220V(rms), 50Hz and has a lagging power factor of 0.7.



- a) [2 marks] Calculate the current, I_s , drawn from the source.

$I_s =$

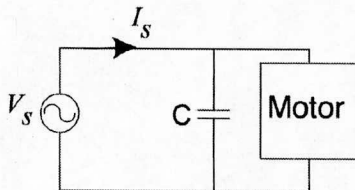- b) [2 marks] The power factor is now increased to 0.95 lagging by placing a capacitor in parallel with the motor as shown. Calculate the new current drawn from the source.




$I_s =$

- c) [6 marks] Determine the value of the capacitor required to make this power factor correction. Illustrate this power factor correction by drawing the corresponding power triangle.

$C =$

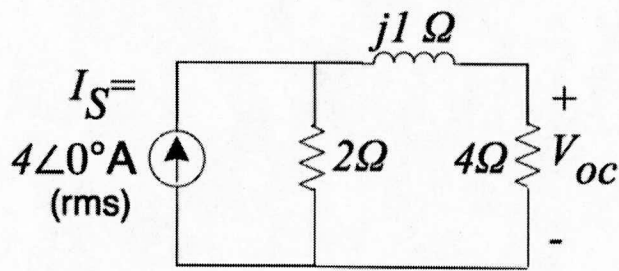QUESTION 3 [5 marks]

Find the voltage V_{oc} in the circuit shown and the complex power, S_S , supplied by current source I_S . Calculate the average power, $P_{4\Omega}$, dissipated by the 4Ω resistor.




$$V_{oc} =$$

$$S_S =$$

$$P_{4\Omega} =$$

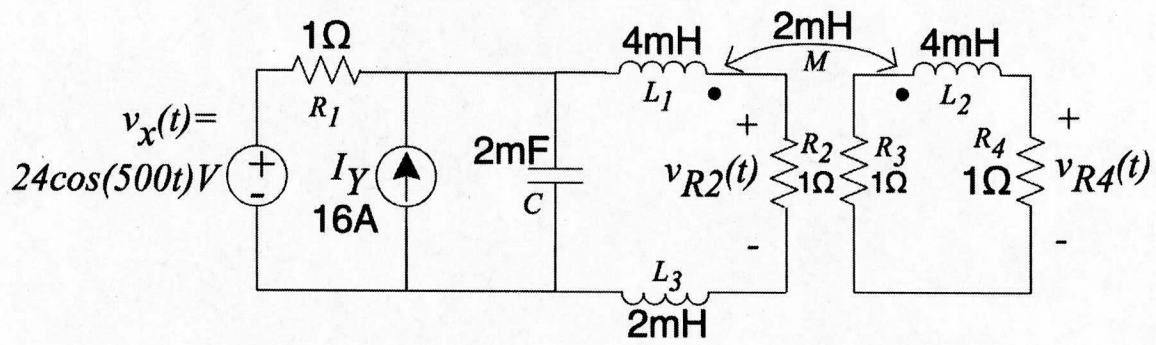QUESTION 4 [10 marks]

The circuit shown below is at steady-state and has both an AC voltage source, $v_x(t)$, and a DC current source, I_Y . Find expressions for voltages $v_{R2}(t)$ and $v_{R4}(t)$ across R_2 and R_4 respectively.




$v_{R2}(t) =$

$v_{R4}(t) =$

QUESTION 4 (blank page for calculations)

QUESTION 5 [5 marks]
Find V_o using nodal analysis.

$V_o =$

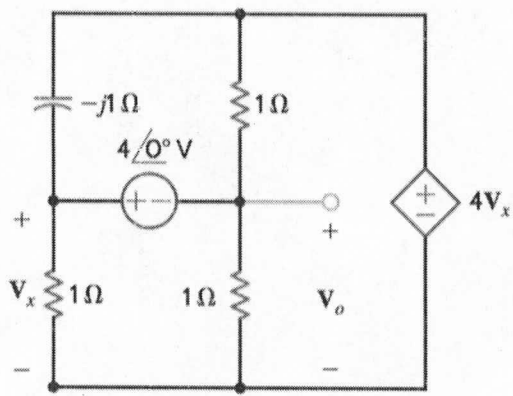


QUESTION 6 [10 marks]

In the circuit shown below, the switch has been in position A for a long time. At time $t=0$, the switch is moved to position B.

a) [8 marks] Find the expression for $i_1(t)$, $i_2(t)$, and $i_3(t)$ for $t \geq 0$.

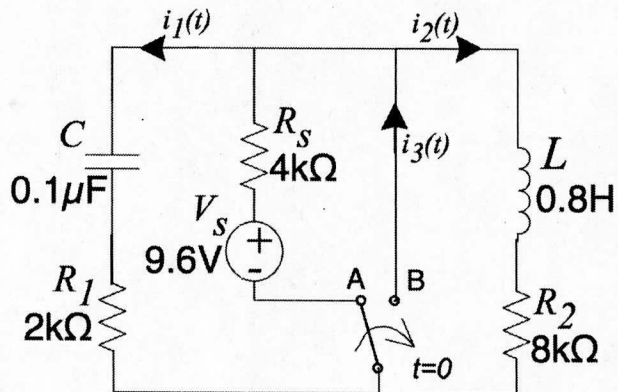b) [2 marks] What is the energy stored in the capacitor, $w_C(0)$, and inductor, $w_L(0)$, at time $t=0$?



$$i_1(t) =$$

$$i_2(t) =$$

$$i_3(t) =$$

$$w_C(0) =$$


$$w_L(0) =$$

QUESTION 6 (blank page for calculations)

QUESTION 7 [10 marks]

Consider the circuit shown below, assuming the op-amp is ideal.

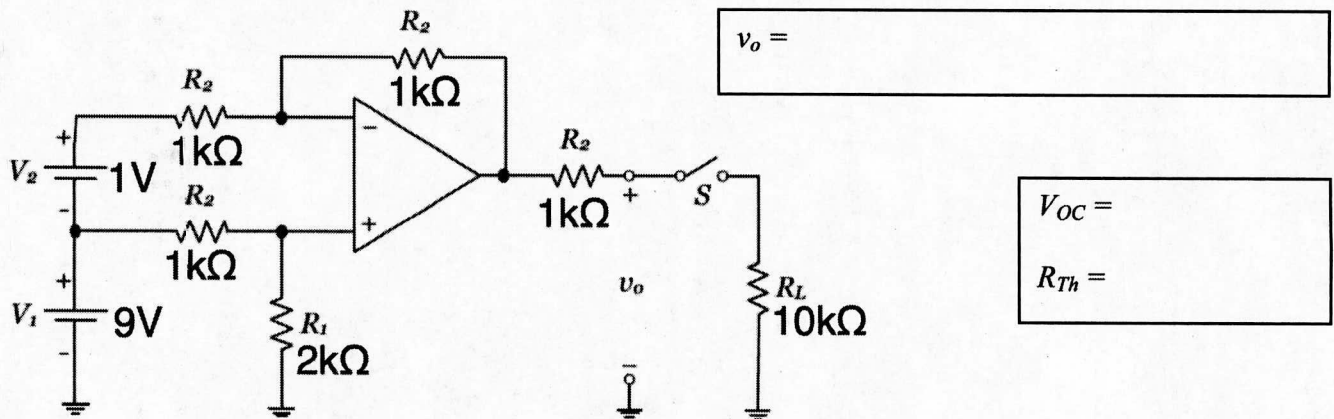- (a) [6 marks] With the switch S in the open position, find an expression for the output voltage v_o in terms of V_1 , V_2 , R_1 and R_2 .
- (b) [4 marks] Find the Thevenin equivalent circuit values, V_{OC} and R_{Th} , seen by the load resistor R_L when the switch S is closed.



(Extra blank page)