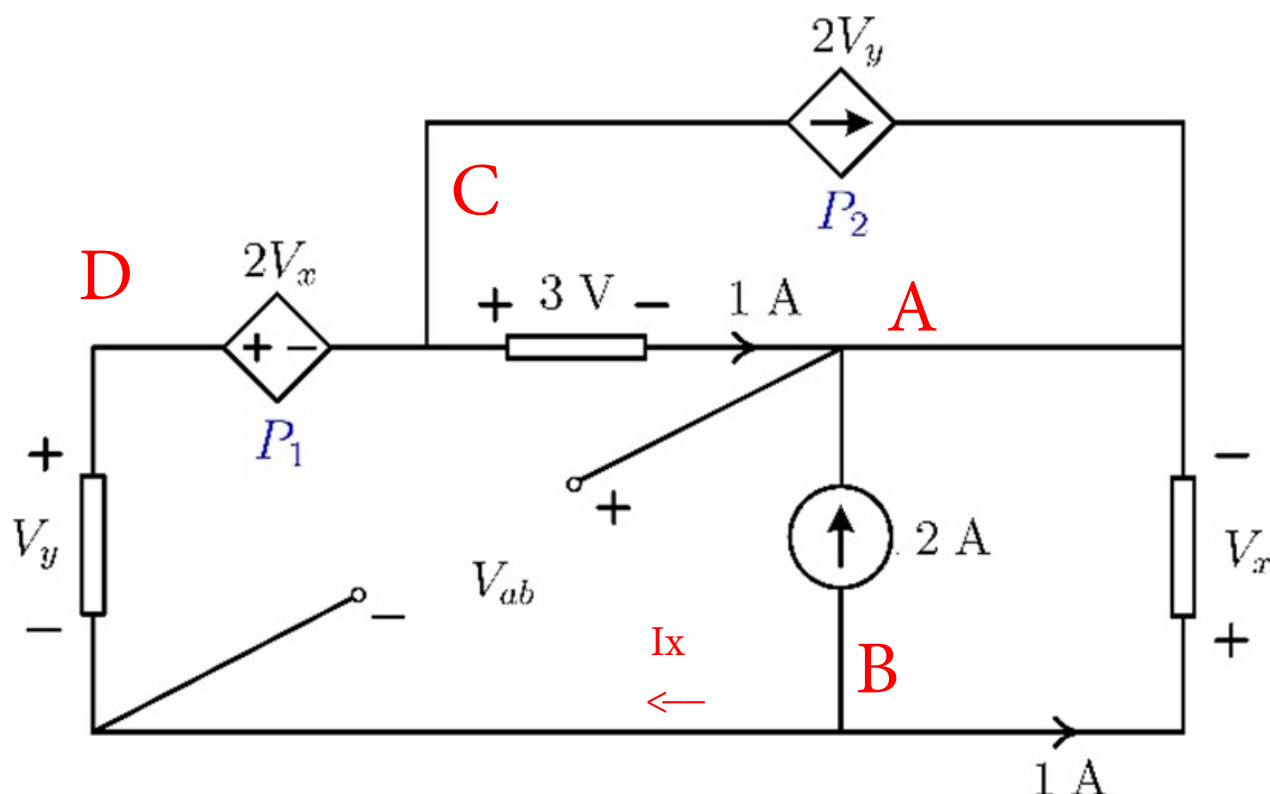


2.

For the circuit below, find the voltage  $V_{ab}$  and the power absorbed by each dependent source ( $P_1$  and  $P_2$  are the powers of the dependent voltage source and dependent current source, respectively).  
[6 points for correct answers, 19 points for process work]

$$\begin{aligned} V_{ab} &= 5.00 \pm 3\% \text{ V} \\ P_1 &= 30.00 \pm 3\% \text{ W} \\ P_2 &= -12.00 \pm 3\% \text{ W} \end{aligned}$$



### KCL @ A

Set current entering node as +

$$1 + 2 + 1 + 2V_y = 0$$

$$V_y = -2$$

$2V_y$  element is in parallel with  $3V$  element, so  $P_2$  is:

$$P_2 = 3V * 2V_y = 3V * (-4A) = -12W$$

$$P_2 = -12W$$

### KVL around D->C->A->B loop

$$-V_y + 2V_x + 3 - V_x = 0$$

$$2 + 2V_x + 3 - V_x = 0$$

$$V_x = -5$$

$$V_{ab} = -V_x = 5$$

$$V_{ab} = 5V$$

### KCL @ B

Set current exiting node as +

$$I_x + 2A + 1A = 0$$

$$I_x = -3A$$

$$P_1 = I_x * 2V_x = -3A * (2 * -5V)$$

$$P_1 = 30W$$